
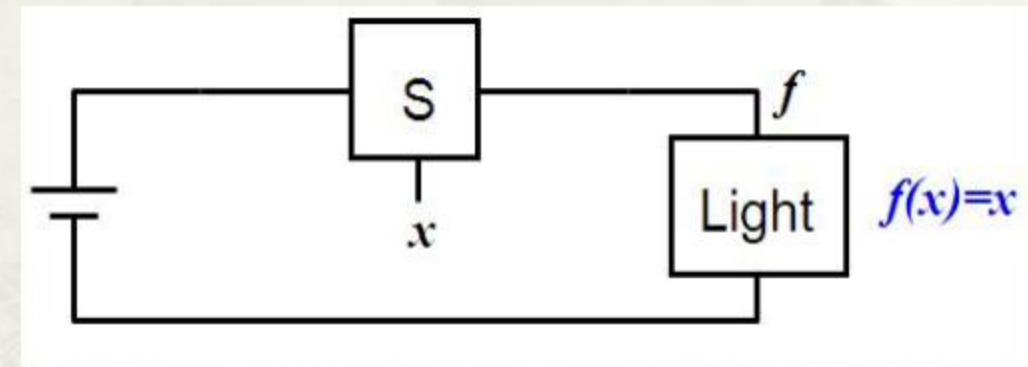


CH2 Fundamental 2: Boolean Algebra

2.1 Variables and Functions

2.1.1 Switch Algebra

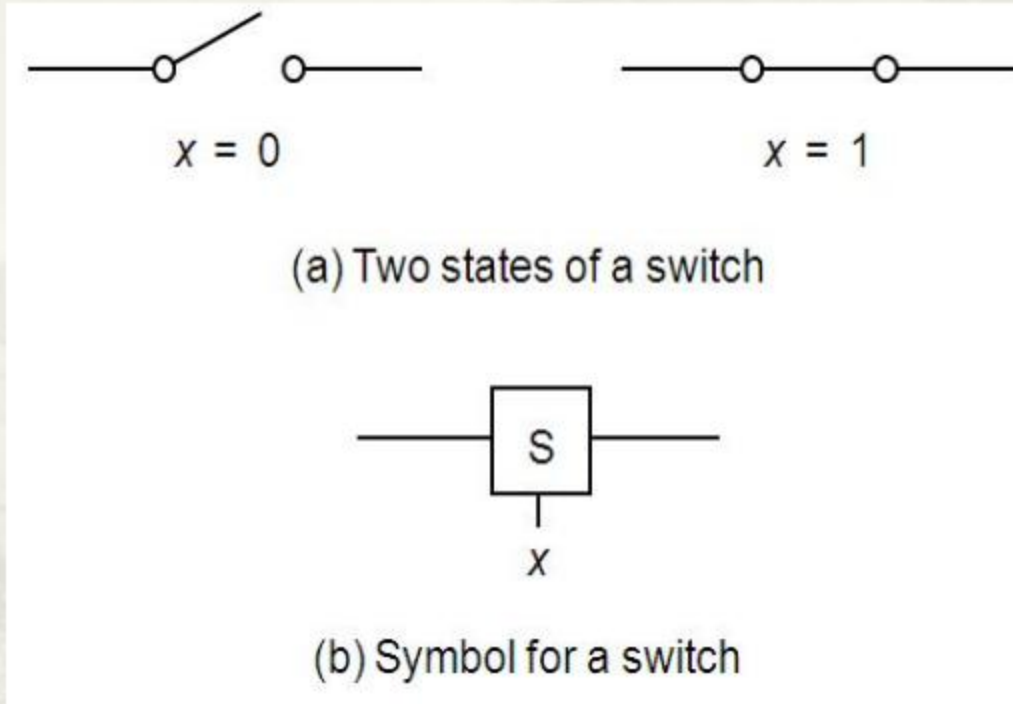


A simple application

2.1.2 Basic Logic Functions(Operations)

- **AND** (logical product)
- **OR** (logical sum)
- **NOT** (Logical complement)

1. AND function

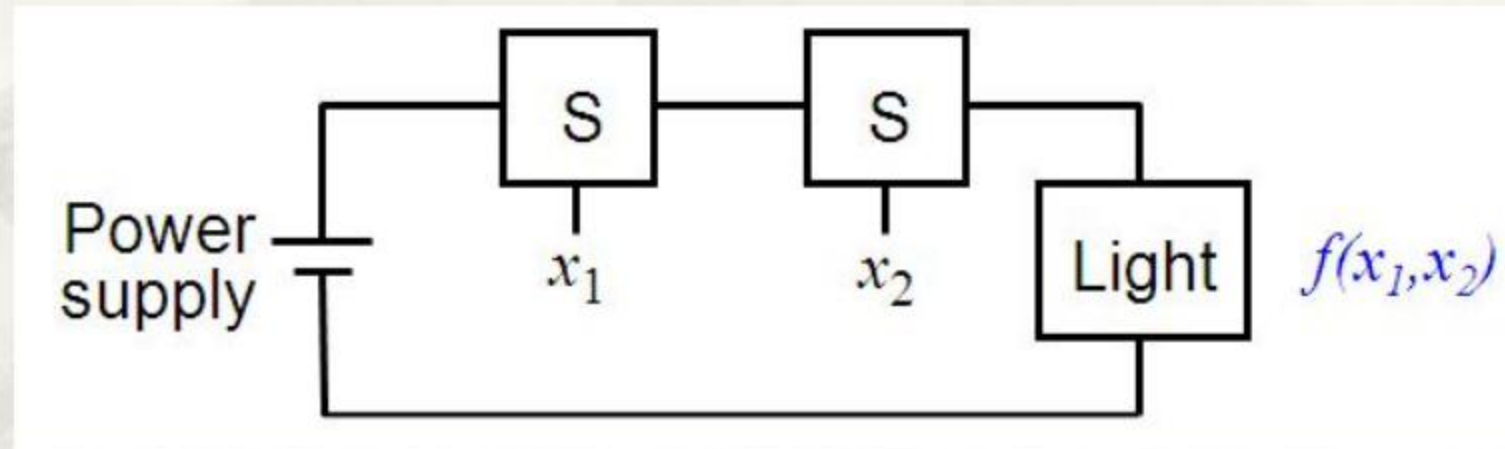


$$f(x_1, x_2) = x_1 \cdot x_2 = x_1 x_2$$

$f=1$ only if $x_1=1$ **AND**
 $x_2=1$, otherwise $f=0$

Logical Product and product term

Note the difference with multiplication

2. OR function

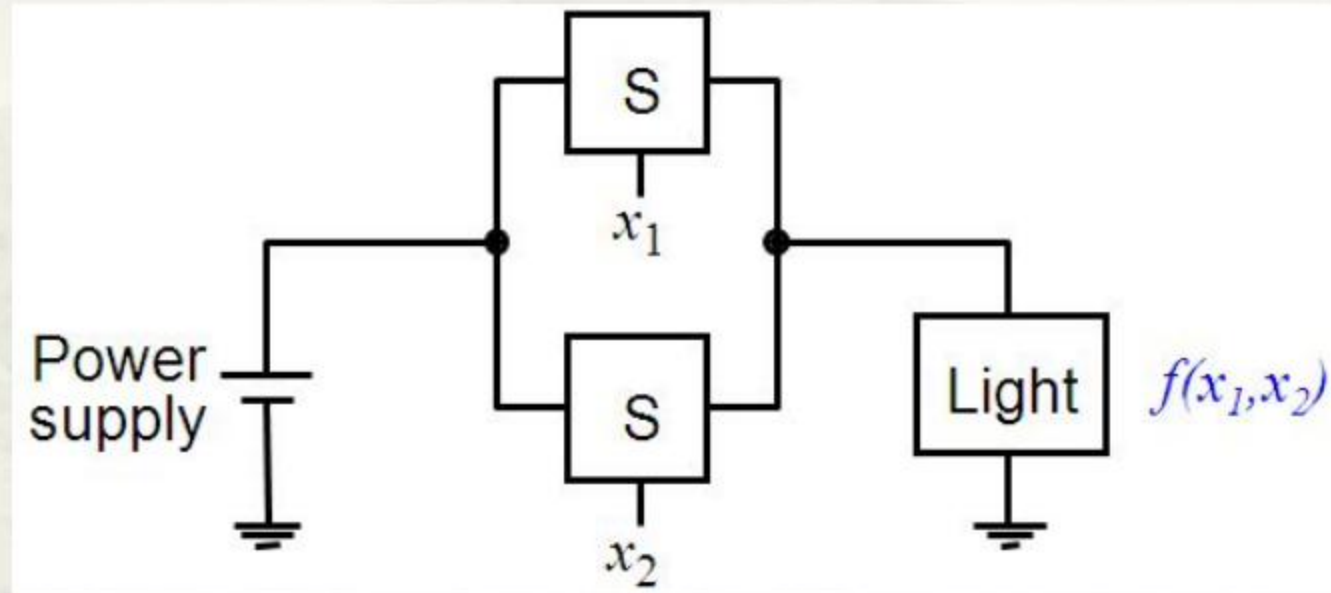


$$f(x_1, x_2) = x_1 + x_2 \quad f=1 \text{ if } x_1=1 \text{ OR } x_2=1,$$

Logical sum and sum term


Note the difference from addition

3. NOT function

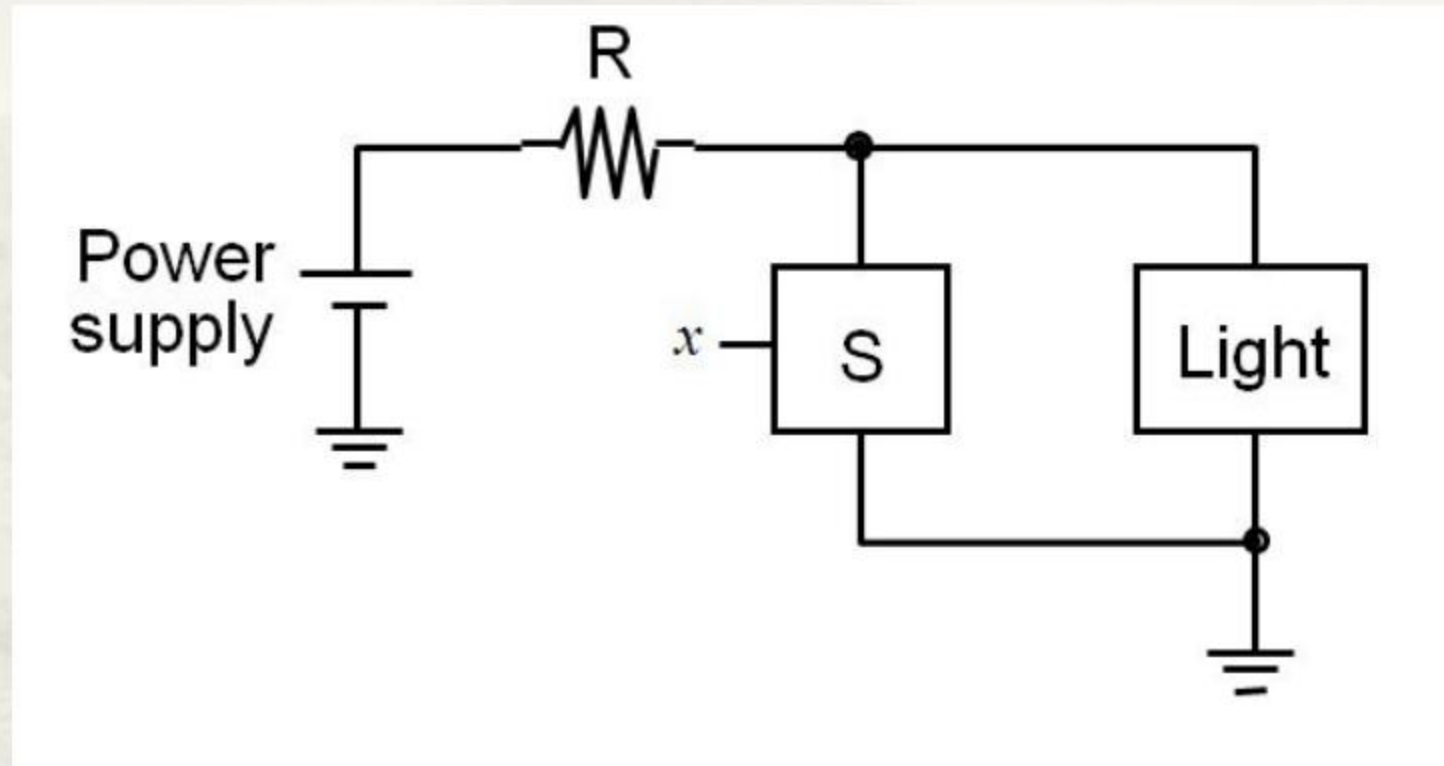

$$f(x) = \bar{x} = NOT\ x = !x = \sim x = x'$$

4. E.g. of Composite Functions

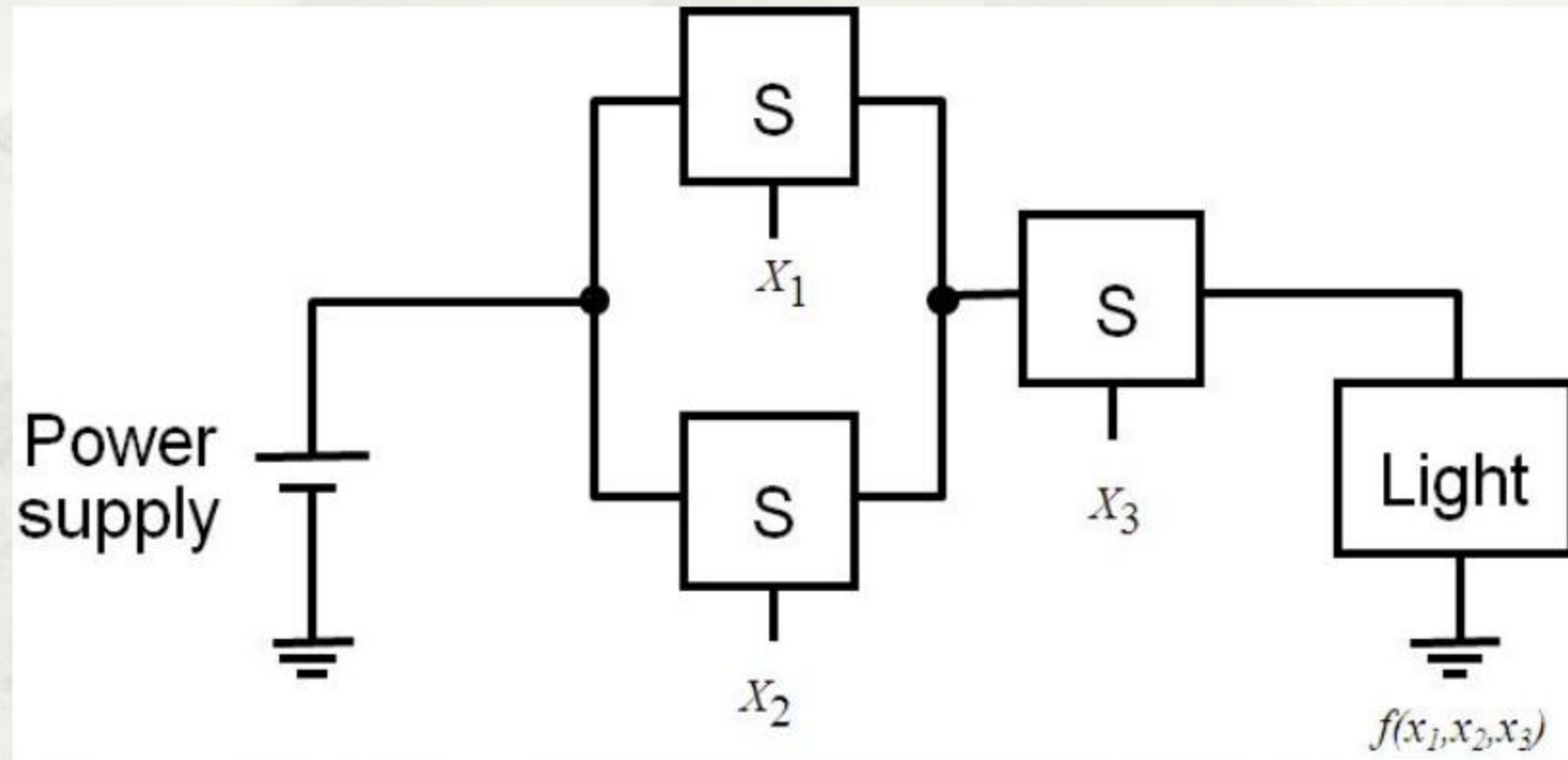

$$f(x_1, x_2, x_3) = (x_1 + x_2)x_3$$

2.2 Truth table for Logic Functions

x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND

OR

2-input AND and OR operations.

x_1	x_2	x_3	$x_1 \cdot x_2 \cdot x_3$	$x_1 \oplus x_2 \oplus x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


3-input AND and OR operations.

Questions:


- Truth table for NOT function?
- Truth table for XOR function?
- Truth table for $f(x_1, x_2, x_3) = (x_1 + x_2)x_3$?

X1	X2	X3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


2.3 Basic Logic Gates

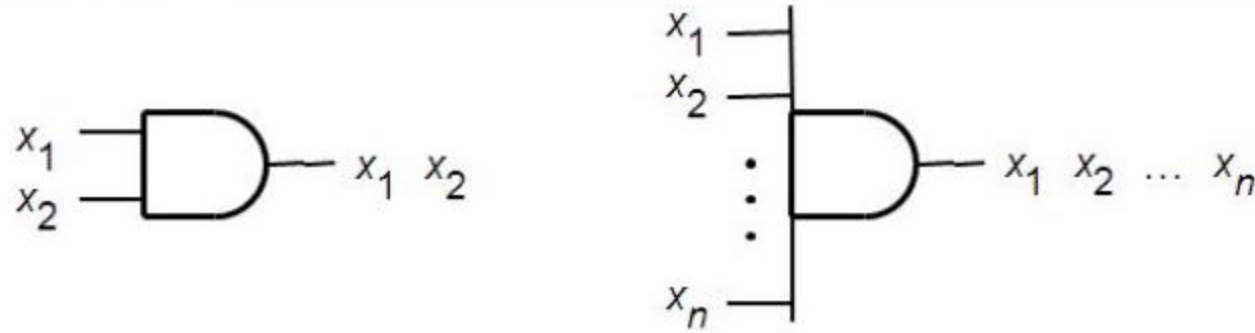

(a) AND gates

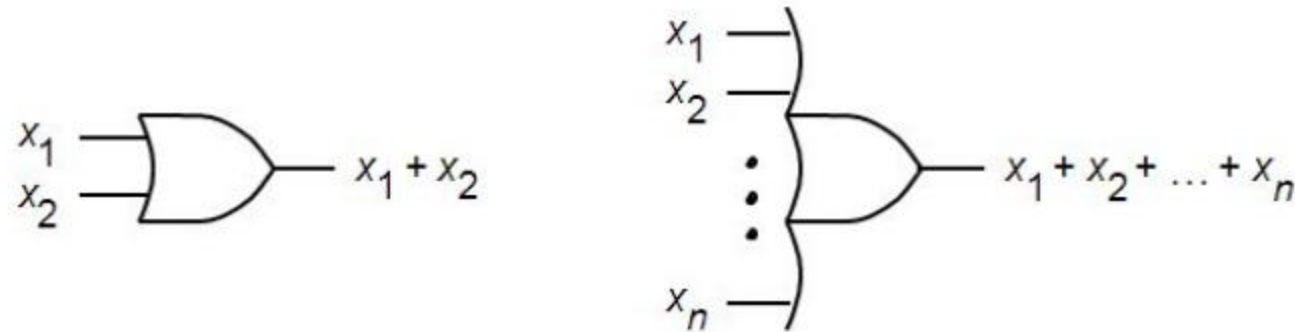

(b) OR gates

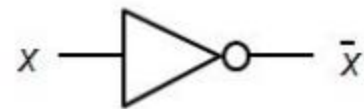

(c) NOT gate

2.4 Rules in Boolean Algebra

2.4.1 Axioms

$$1a. 0 \cdot 0 = 0$$

$$1b. 1 + 1 = 1$$

$$2a. 1 \cdot 1 = 1$$

$$2b. 0 + 0 = 0$$

$$3a. 0 \cdot 1 = 1 \cdot 0 = 0$$

$$3b. 1 + 0 = 0 + 1 = 1$$

$$4a. \text{ if } x = 0 \boxtimes \bar{x} = 1$$

$$4b. \text{ if } x = 1 \boxtimes \bar{x} = 0$$

2.4.2 Single-Variable Theorems

$$5a. x \cdot 0 = 0$$

$$5b. x + 1 = 1$$

$$6a. x \cdot 1 = x$$

$$6b. x + 0 = x$$

$$7a. x \cdot x = x$$

$$7b. x + x = x$$

$$8a. x \cdot \bar{x} = 0$$

$$8b. x + \bar{x} = 1$$

$$9. \bar{\bar{x}} = x$$

2.4.3 2- and 3-Variable ones

$$10a. xy = yx$$

Commutative

$$10b. x + y = y + x$$

$$11a. x(yz) = (xy)z$$

Associative

$$11b. x + (y + z) = (x + y) + z$$

$$12a. x(y + z) = xy + xz$$

Distributive

$$12b. \underline{x + yz = (x + y)(x + z)}$$

$$13a. \underline{x + xy = x}$$

Absorption

$$13b. x(x + y) = x$$

$$14a. \underline{x + \bar{x}y = x + y}$$

$$14b. x(\bar{x} + y) = xy$$

2.4.3 2- and 3-Variable Identities

$$15a. \ xy + x\bar{y} = x$$

Combining

$$15b. \ (x + y)(x + \bar{y}) = x$$

$$16a. \ \underline{\overline{xy} = \bar{x} + \bar{y}}$$

DeMorgan's theorem

$$16b. \ \overline{x + y} = \bar{x} \cdot \bar{y}$$

$$17a. \ \underline{xy + \bar{x}z + yz = xy + \bar{x}z}$$

Consensus

$$17b. \ (x + y)(\bar{x} + z)(y + z) = (x + y)(\bar{x} + z)$$

Simple applications

$$1. \bar{A}\bar{B} + B + BCD$$

$$= A + B + BCD$$

$$= A + B$$

Absorption

Absorption

$$2. AB + \bar{A} \cdot \bar{B}C + BC$$

$$= AB + C(\bar{A} \cdot \bar{B} + B)$$

Distributive and Commutative

$$= AB + C(\bar{A} + B)$$

Absorption

$$= AB + \bar{A}C + BC$$

Distributive

$$= AB + \bar{A}C$$

Consensus

2.4.4 Other theorems

1. DeMorgan's theorem

$$(1) \quad \overline{X_1 + X_2 + \dots + X_n} = \overline{X_1} \cdot \overline{X_2} \cdot \dots \cdot \overline{X_n}$$

$$(2) \quad \overline{X_1 \cdot X_2 \cdot \dots \cdot X_n} = \overline{X_1} + \overline{X_2} + \dots + \overline{X_n}$$

2. Theorem of Duality

If $F = f(x_1, x_2, \dots, x_n, 0, 1, +, \cdot)$

then $F_d = f(x_1, x_2, \dots, x_n, 1, 0, \cdot, +)$

The order of operations must be UNCHANGED!

e.g.:

$$F = \bar{A}B + A\bar{B}\bar{C}$$

$$F_d = (\bar{A} + B)(A + \bar{B} + \bar{C})$$

$$F = A(\bar{B} + CD) + E$$

$$F_d = [A + \bar{B}(C + D)]E$$

$$F = (A + 0)(B + C \cdot 1) \quad F_d = A \cdot 1 + B(C + 0)$$

$$F = A + B + \bar{C} + \bar{D} + \bar{E}$$

$$F_d = A \cdot B \cdot \bar{C} \cdot \bar{D} \cdot \bar{E}$$

Exercise: find the dual of $F = \bar{A}B + A\bar{B} \cdot (C + \bar{D})$

$$F_d = (\bar{A} + B) \cdot (A + \bar{B} + C\bar{D})$$

3. Theorem of inverse functions

If $F = f(x_1, x_2, \dots, x_n, 0, 1, +, \cdot)$
then $\overline{F} = f(\overline{x_1}, \overline{x_2}, \dots, \overline{x_n}, 1, 0, \cdot, +)$

e.g.:

$$F(A, B, C, D) = \bar{A} + B(\bar{C} + D)$$

$$F = \bar{A}B + A\bar{B}\bar{C}$$

$$\bar{F} = (A + \bar{B})(\bar{A} + B + C)$$

$$F = A(\bar{B} + CD) + E$$

$$\bar{F} = [\bar{A} + B(\bar{C} + \bar{D})] \bar{E}$$

$$F = (A + 0)(B + C \cdot 1)$$

$$\bar{F} = \bar{A} \cdot 1 + \bar{B}(\bar{C} + 0)$$

$$F = A + B + \overline{\overline{\overline{\bar{C}} + \bar{D} + \bar{E}}}$$

$$\bar{F} = \bar{A} \cdot \bar{B} \cdot \overline{\overline{\overline{\bar{C}} \cdot \bar{D} \cdot \bar{E}}}$$

Exercise: find the inverse of $F = \bar{A}B + A\bar{B}(C + \bar{D})$

$$\bar{F} = (A + \bar{B})(\bar{A} + B\bar{C}\bar{D})$$

2.5 General Forms of Logic functions:

Sum-of-Products(SOP) and **Product-of-Sums(POS)**

2.5.1 SOP: AND-OR

- A function in form of the truth table

x_1	x_2	$f(x_1, x_2)$	
0	0	1	← $\overline{x_1}\overline{x_2}$
0	1	1	← $\overline{x_1}x_2$
1	0	0	
1	1	1	← x_1x_2

$$f(x_1, x_2) = \overline{x_1}\overline{x_2} + \overline{x_1}x_2 + x_1x_2$$

Minterms

- A minterm is a **product term** in which **each** of variables appears **once and only once**, either in uncomplemented or complemented form.

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

← $\overline{x_1}\overline{x_2}$

← $\overline{x_1}x_2$

← x_1x_2

Simplified representation for minterms

- m_i : i is determined by:
 - Fixing the order of variables
 - Writing 0 for $\bar{x}$
 - Writing 1 for x
 - i is the decimal value of the sequence.

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

← $\bar{x}_1\bar{x}_2$ m_0
← $\bar{x}_1x_2$ m_1
← x_1x_2 m_3

$$f(x_1, x_2) = m_0 + m_1 + m_3 = \sum m(0, 1, 3)$$

Canonical SOP form

'i' is also determined by the row number!

Canonical SOP

- The canonical SOP form consists of only minterms.
- How to find the canonical SOP given an arbitrary expression?
$$F(A, B, C) = \bar{A}B + A\bar{B}\bar{C} + BC$$
- E.g.:

What's more...

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

← $\overline{x_1}\overline{x_2}$ m_0

← $\overline{x_1}x_2$ m_1

← x_1x_2 m_3

$$\begin{aligned}f(x_1, x_2) &= \overline{x_1}\overline{x_2} + \overline{x_1}x_2 + x_1x_2 \\&= \overline{x_1}(\overline{x_2} + x_2) + x_1x_2 \\&= \overline{x_1} + x_1x_2 \\&= \overline{x_1} + x_2\end{aligned}$$

Canonical SOP

Non-SOP

SOP

Minimum-cost SOP

Another example

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$\begin{aligned}f(x_1, x_2, x_3) &= \overline{x_1}\overline{x_2}x_3 + x_1\overline{x_2}\overline{x_3} + x_1\overline{x_2}x_3 + x_1x_2\overline{x_3} \\ &= \sum m(1, 4, 5, 6)\end{aligned}$$

Three-variable minterms

Row number	x_1	x_2	x_3	Minterm
0	0	0	0	$m_0 = \overline{x}_1 \overline{x}_2 \overline{x}_3$
1	0	0	1	$m_1 = \overline{x}_1 \overline{x}_2 x_3$
2	0	1	0	$m_2 = \overline{x}_1 x_2 \overline{x}_3$
3	0	1	1	$m_3 = \overline{x}_1 x_2 x_3$
4	1	0	0	$m_4 = x_1 \overline{x}_2 \overline{x}_3$
5	1	0	1	$m_5 = x_1 \overline{x}_2 x_3$
6	1	1	0	$m_6 = x_1 x_2 \overline{x}_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$

2.5.2 POS: OR-AND

- A function in the form of truth table

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$$\boxtimes \bar{f} = m_2$$

$$\therefore f = \overline{m_2} = \overline{x_1 x_2} = (\overline{x_1} + \overline{x_2})$$

$$\overline{x_1} \overline{x_2}$$

$$\overline{x_1} x_2$$

$$\overline{m_2} = \overline{x_1 x_2} = \overline{x_1} + \overline{x_2}$$

$$x_1 x_2$$

Maxterms

- A maxterm is a sum term in which **each** of variables appears once and only once, either in uncomplemented or complemented form.
- **M_i** : i is determined by:
 - Fix the order of variables
 - Write 1 for x
 - Write 0 for $\bar{x}$
 - i is the decimal value of the sequence.
- i is also indicated by the row number.

i is also indicated by the row number.

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

← M_2

$$f = \overline{m}_2 = \overline{x_1 x_2} = \overline{x_1} + x_2 = M_2$$

Another example

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$\bar{f}(x_1, x_2, x_3) = m_0 + m_2 + m_3 + m_7$$

$$\therefore f(x_1, x_2, x_3) = \overline{m_0 + m_2 + m_3 + m_7}$$

$$= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_7}$$

$$= M_0 \cdot M_2 \cdot M_3 \cdot M_7$$

$$= (x_1 + x_2 + x_3)(x_1 + \overline{x_2} + x_3)(x_1 + \overline{x_2} + \overline{x_3})(\overline{x_1} + \overline{x_2} + \overline{x_3})$$

$$= \prod M(0, 2, 3, 7) \quad \text{Canonical POS}$$

Canonical POS form

- The POS form consists of only maxterms.



What's more...

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \prod M(0, 2, 3, 7)$$

= ...

$$= (x_1 + x_3)(\overline{x_2} + \overline{x_3})$$

Minimum-cost POS

Given $F(A, B, C) = \bar{A}B + A\bar{B}\bar{C} + BC$ **Find its canonical POS.**

$$\begin{aligned} F(A, B, C) &= (\bar{A}B + A) (\bar{A}B + \bar{B}) (\bar{A}B + \bar{C}) + BC \\ &= (\bar{A} + A) (B + A) (\bar{A} + \bar{B}) (B + \bar{B}) (\bar{A} + \bar{C}) \\ &\quad (B + \bar{C}) + BC \\ &= (A + B) (\bar{A} + \bar{B}) (\bar{A} + \bar{C}) (B + \bar{C}) + BC \\ &= ((A + B) (\bar{A} + \bar{B}) (\bar{A} + \bar{C}) (B + \bar{C}) + B) \\ &\quad \cdot ((A + B) (\bar{A} + \bar{B}) (\bar{A} + \bar{C}) (B + \bar{C}) + C) \\ &= ((A + B + B) (\bar{A} + \bar{B} + B) (\bar{A} + \bar{C} + B) (B + \bar{C} + B)) \\ &\quad \cdot ((A + B + C) (\bar{A} + \bar{B} + C) (\bar{A} + \bar{C} + C) (B + \bar{C} + C)) \\ &= (A + B) (\bar{A} + B + \bar{C}) (B + \bar{C}) (A + B + C) (\bar{A} + \bar{B} + C) \\ &= (A + B + C\bar{C}) (\bar{A} + B + \bar{C}) (A\bar{A} + B + \bar{C}) (A + B + C) (\bar{A} + \bar{B} + C) \\ &= (A + B + C) (A + B + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + C) \\ &\quad \begin{array}{cccccccccccc} \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 1 & 1 & 1 & 0 \end{array} \\ &= \Pi M(0, 1, 5, 6) \end{aligned}$$

What do you think of the algebraic approach?

Review previous examples and seek a shortcut

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$\bar{f}(x_1, x_2, x_3) = m_0 + m_2 + m_3 + m_7$$

$$\therefore f(x_1, x_2, x_3) = \overline{m_0 + m_2 + m_3 + m_7}$$

$$= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_7}$$

$$= M_0 \cdot M_2 \cdot M_3 \cdot M_7$$

$$= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3)$$

$$= \prod M(0, 2, 3, 7) \quad \text{Canonical POS}$$

Questions:

- Relationship between canonical SOP and canonical POS?

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$\begin{aligned} f(x_1, x_2, x_3) &= \sum m(1, 4, 5, 6) \\ &= \prod M(0, 2, 3, 7) \end{aligned}$$

Three-variable minterms and maxterms.

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

2.6 Finding the minimum-cost functions: algebraic approach

$$13a. x + xy = x$$

Absorption

$$13b. x(x + y) = x$$

$$14a. x + \bar{x}y = x + y$$

$$14b. x(\bar{x} + \underline{y}) = xy$$

$$15a. xy + x\bar{y} = x$$

Combining

$$15b. (x + y)(x + \bar{y}) = x$$

$$16a. \overline{xy} = \bar{x} + \bar{y}$$

DeMorgan's theorem

$$16b. \overline{x + y} = \bar{x} \cdot \bar{y}$$

$$17a. xy + \bar{x}z + yz = xy + \bar{x}z$$

Consensus

$$17b. (x + y)(\bar{x} + z)(y + z) = (x + y)(\bar{x} + z)$$

E.g.:

□ 1.

$$A\bar{B}C + A\bar{B}\bar{C} = A\bar{B}$$

$$AB\bar{C} + A\bar{B}\bar{C} = A$$

□ 2.

$$\bar{B} + A\bar{B}D = \bar{B}$$

$$\bar{A}B + \bar{A}BCD(E+F) = \bar{A}B$$

□ 3.

$$\begin{aligned} AB + \bar{A}C + \bar{B}C &= AB + (\bar{A} + \bar{B})C \\ &= AB + \bar{A}\bar{B}C \\ &= AB + C \end{aligned}$$

E.g.:

□ 4. a more difficult one

$$\begin{aligned} A\bar{B} + B\bar{C} + \bar{B}C + \bar{A}B &= A\bar{B} + B\bar{C} + (\underline{A + \bar{A}}) \bar{B}C + \bar{A}B (\underline{C + \bar{C}}) \\ &= \underline{A\bar{B}} + \underline{B\bar{C}} + \underline{A\bar{B}C} + \underline{\bar{A}\bar{B}C} + \underline{\bar{A}BC} + \underline{\bar{A}B\bar{C}} \\ &= A\bar{B} + B\bar{C} + \bar{A}C \end{aligned}$$

Exercises:

1. $F = A\bar{C} + ABC + AC\bar{D} + CD$
2. $F = AD + A\bar{D} + AB + \bar{A}C + BD + ACEF + \bar{B}EF + DEFG$
3. $F = BC + D + \bar{D}(\bar{B} + \bar{C})(AC + B)$

2.7 Karnaugh Map

- Truth table in essence.
- Matrix: 2D truth table.
- Variables divided into 2 groups arbitrarily.
- Values **in gray-code arrangement** for every group .
- Every **cell** in K-map corresponds to every row in truth table.

2.7.1 Comparison between truth table and K-map

x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

(a) Truth table

		x_1	
		0	1
x_2	0	m_0	m_2
	1	m_1	m_3

(b) Karnaugh map

2.7.2 Adjacency of minterms

- For any n -variable function's minterm/maxterm, there are n adjacent minterms/maxterms.

		x_1	
		0	1
x_2	0	m_0	m_2
	1	m_1	m_3

2-variable
K-map

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

3-variable
K-map

2.7.2 Adjacency of terms: continue

- For an n -variable function's minterm/maxterm, there are n adjacent minterms/maxterms.


$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
00	m_0	m_4	m_{12}	m_8	
01	m_1	m_5	m_{13}	m_9	
11	m_3	m_7	m_{15}	m_{11}	
10	m_2	m_6	m_{14}	m_{10}	

4-variable
K-map

2.7.3 Denoting a function by K-map

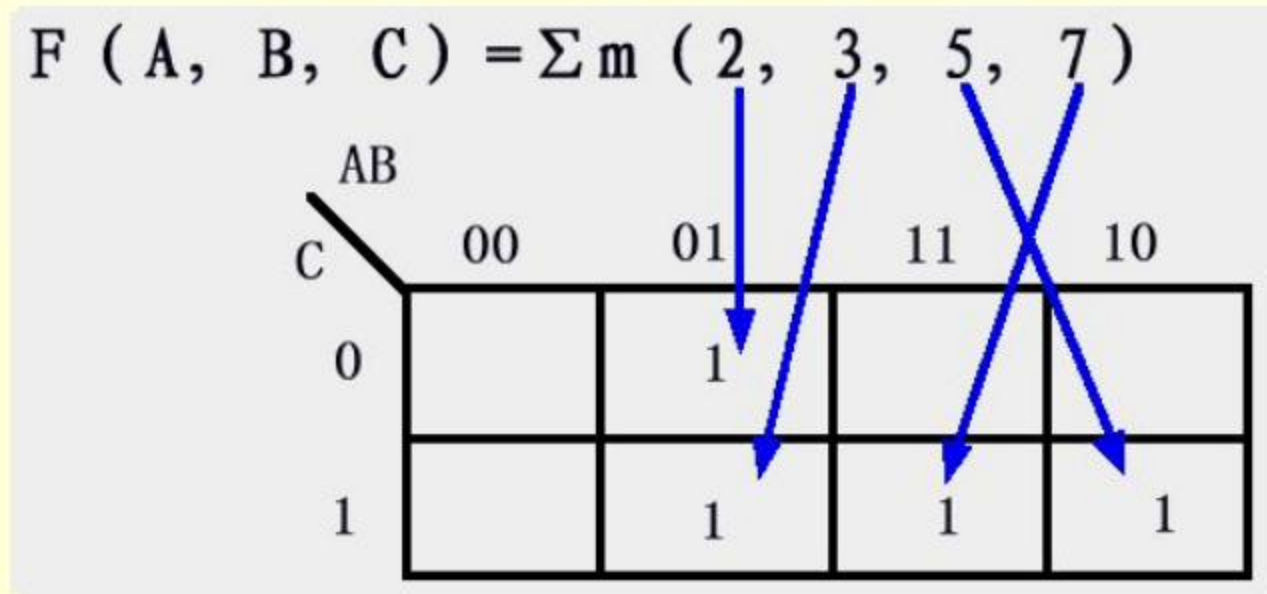1. Canonical SOP

- Fill every cell with '**1**' corresponding to every minterm.
- E.g.:



- A minterm corresponds to a cell filled with 1.

2.7.3 Denoting a function by K-map

2. General SOP

- Fill cells with '**1s**' corresponding to every product term.
- E.g.:

$F(A, B, C) = AB + A\bar{C}$

$C \backslash AB$	00	01	11	10
0			1	1
1			1	

- A product term corresponds to a group of cells filled with 1s.

2.7.3 Denoting a function by K-map

3. Canonical POS

- Fill every cell with '0' corresponding to every maxterm.
- E.g.: $F(x_1, x_2, x_3, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15)$

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	1	1	0	1
10	1	1	1	1

- A maxterm corresponds to a cell filled with 0.

2.7.3 Denoting a function by K-map

4. General POS

- Fill cells with '**0s**' corresponding to every sum term.

□ E.g.:

$$F(x_1, x_2, x_3) = (\overline{x_1} + x_3)(\overline{x_1} + x_2)$$


$x_3 \backslash x_1 x_2$	00	01	11	10
0	1	1	0	0
1	1	1	1	0

- A sum term corresponds to a group of cells filled with 0s.




2.7.4 Key features of K-map

- **2^i adjacent 1s** can be merged into a single **product term**, from which **i variables are dropped**.
- 2^i adjacent 0s can be merged into a single *sum term*, from which i variables are dropped.


Cases of 2 adjacent 1s

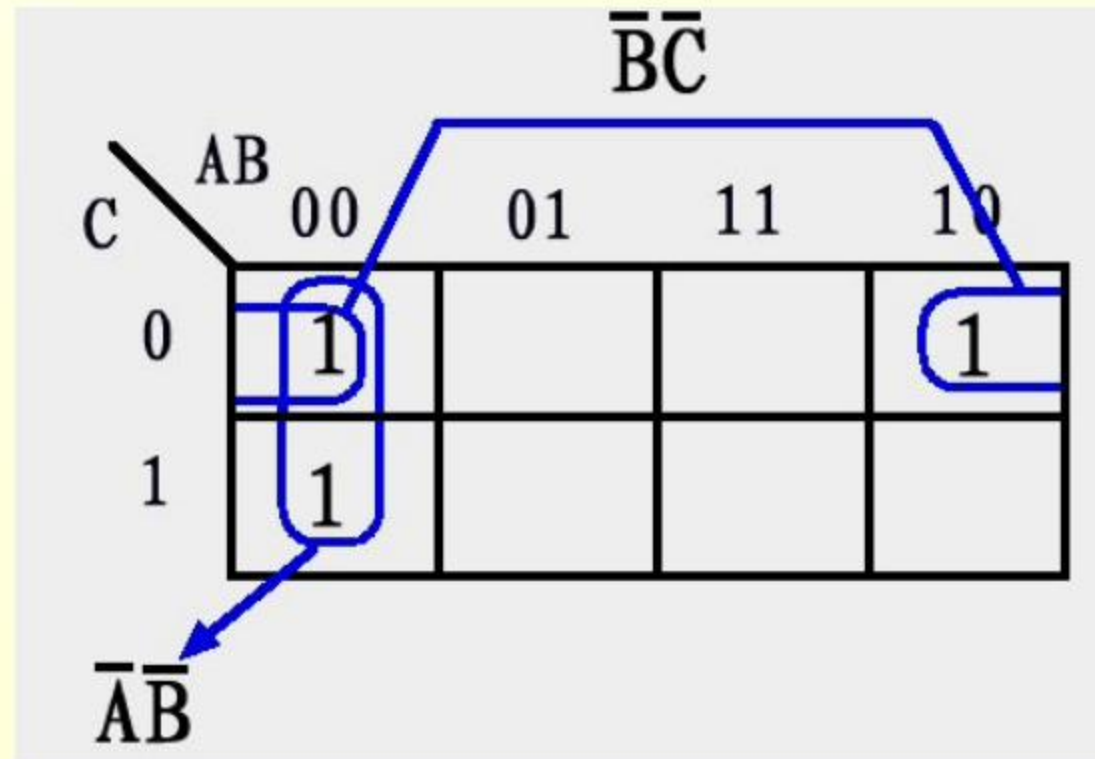

Cases of 4 adjacent 1s

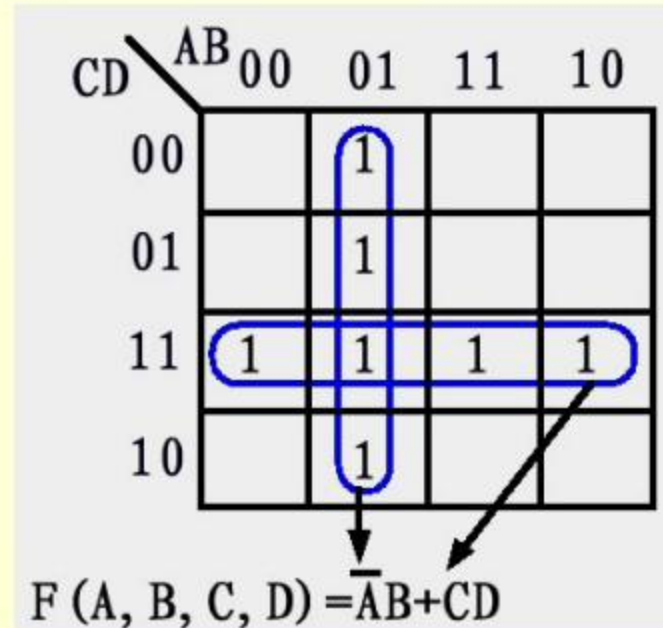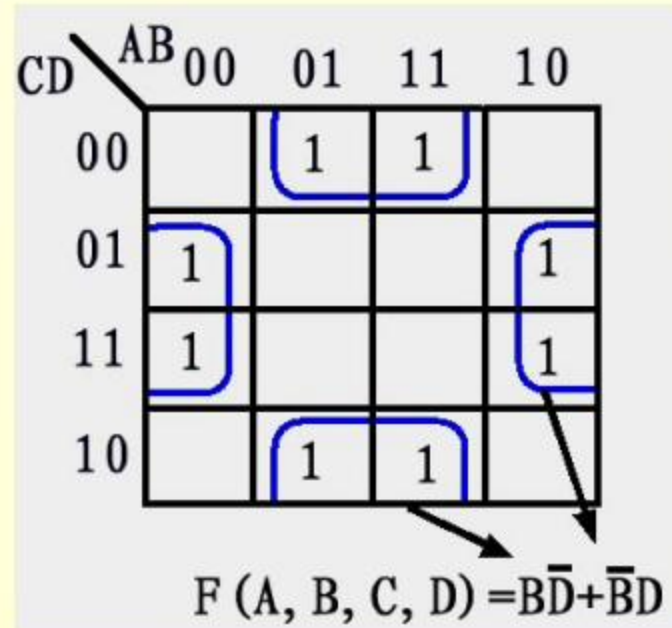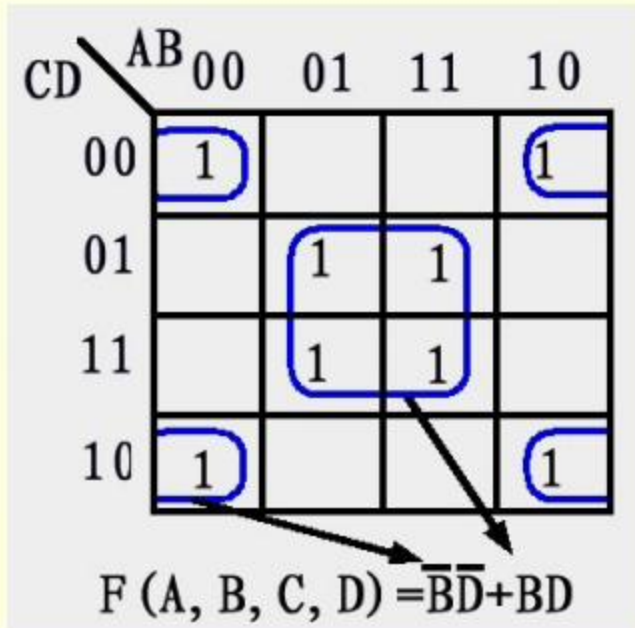

Cases of 8 adjacent 1s

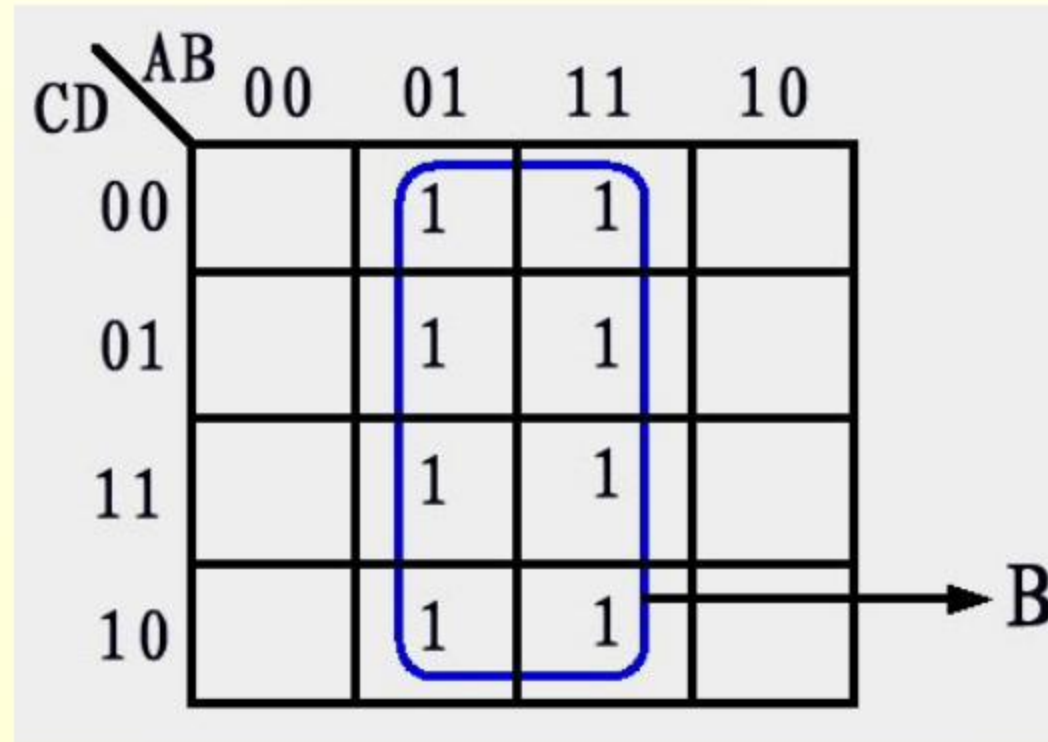

CD \ AB	00	01	11	10
00		1	1	
01		1	1	
11		1	1	
10		1	1	


2.7.5 Strategy for Minimization

1. Finding the simplest SOP with K-map


- Cover all 1s.
- 2^i adjacent 1s in every circle.
- Find as fewer groups to cover all 1s as possible(High priority)
 - *The fewer the groups ,the fewer product terms in the expression*
- Find every group(a circle) covering as many 1s as possible.
 - *The larger the group, the fewer variables in the corresponding product term.(Low priority)*

Examples

▣ **1.** $F(x_1, x_2) = \sum m(0, 1, 3)$

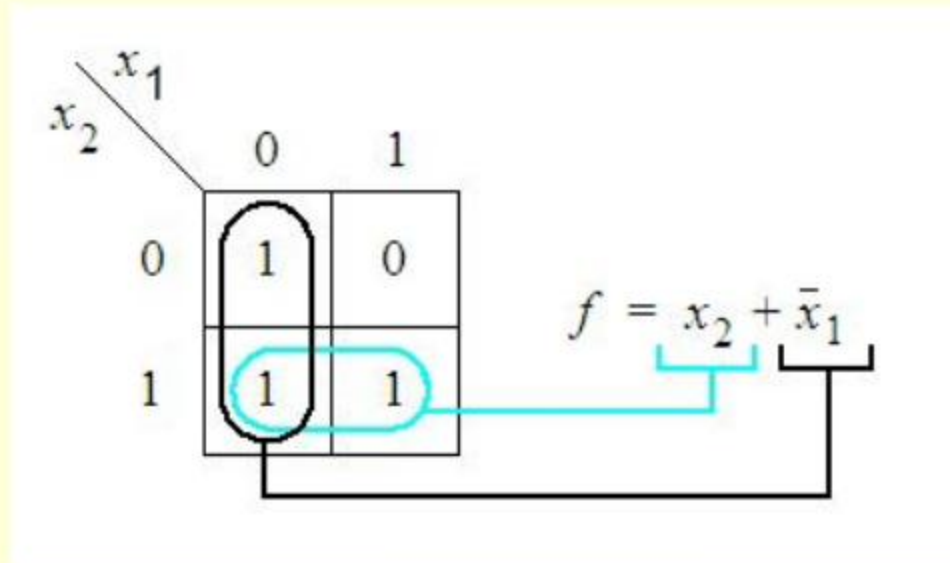


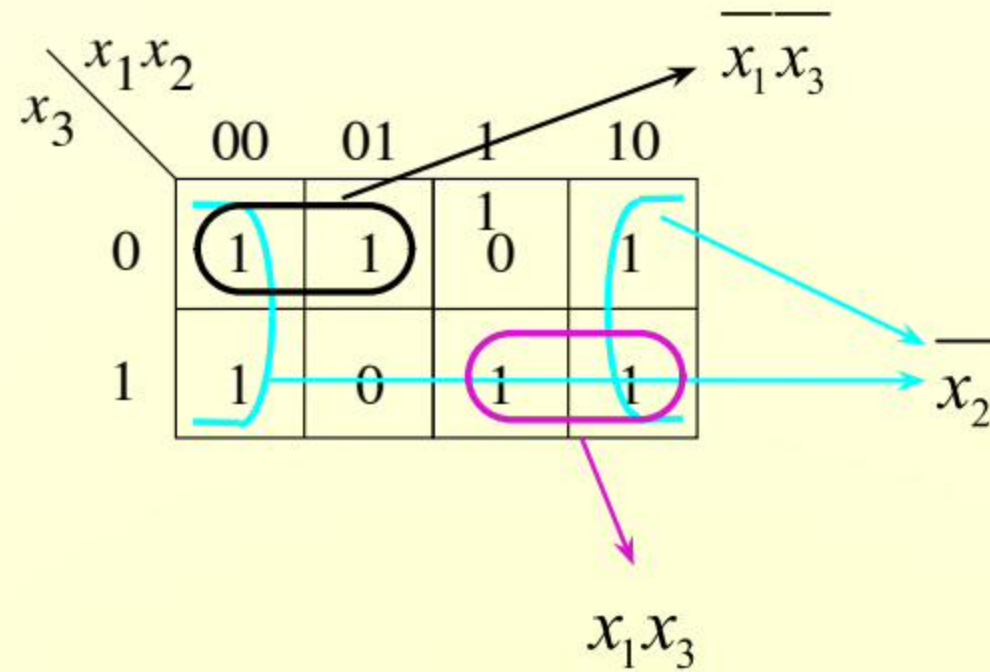▣ **2.** $F(x_1, x_2, x_3) = \sum m(0, 1, 2, 4, 5, 7)$



$$F(x_1, x_2, x_3) = \overline{x_2} + \overline{x_1}\overline{x_3} + x_1x_3$$

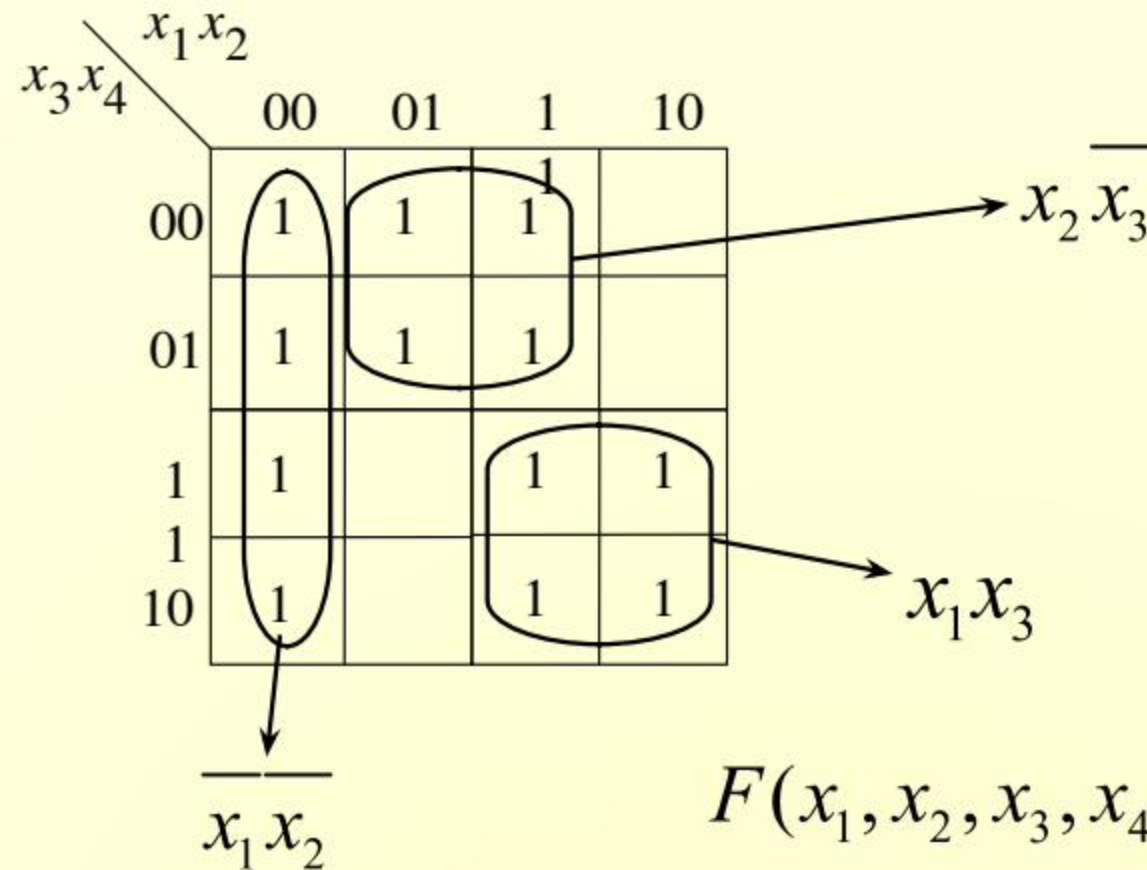3. $F(x_1, x_2, x_3, x_4) = \overline{\overline{x_1} \overline{x_2}} + \overline{\overline{x_1} x_3 x_4} + x_1 x_3 + x_2 \overline{x_3}$



Another solution?

$$F(x_1, x_2, x_3, x_4) = \overline{\overline{x_1} \overline{x_2}} + x_2 \overline{x_3} + x_1 x_3$$

Exercises

$$F(A, B, C) = A\overline{B} + B\overline{C} + \overline{B}C + \overline{A}B$$

$$F(A, B, C, D) = \sum m(0, 3, 4, 5, 7, 11, 13, 15)$$


$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 6, 7, 8, 9, 11, 15)$$

2. Finding the simplest POS using K-map

- Cover all 0s.
- Cover 2^i adjacent 0s one time.
- Find every group(a circle) covering as many 0s as possible.
 - *The larger the group, the fewer variables in the corresponding sum term.*
- Find as few groups to cover all 0s as possible
 - *The fewer the groups, the fewer sumterms in the expression.*

Examples

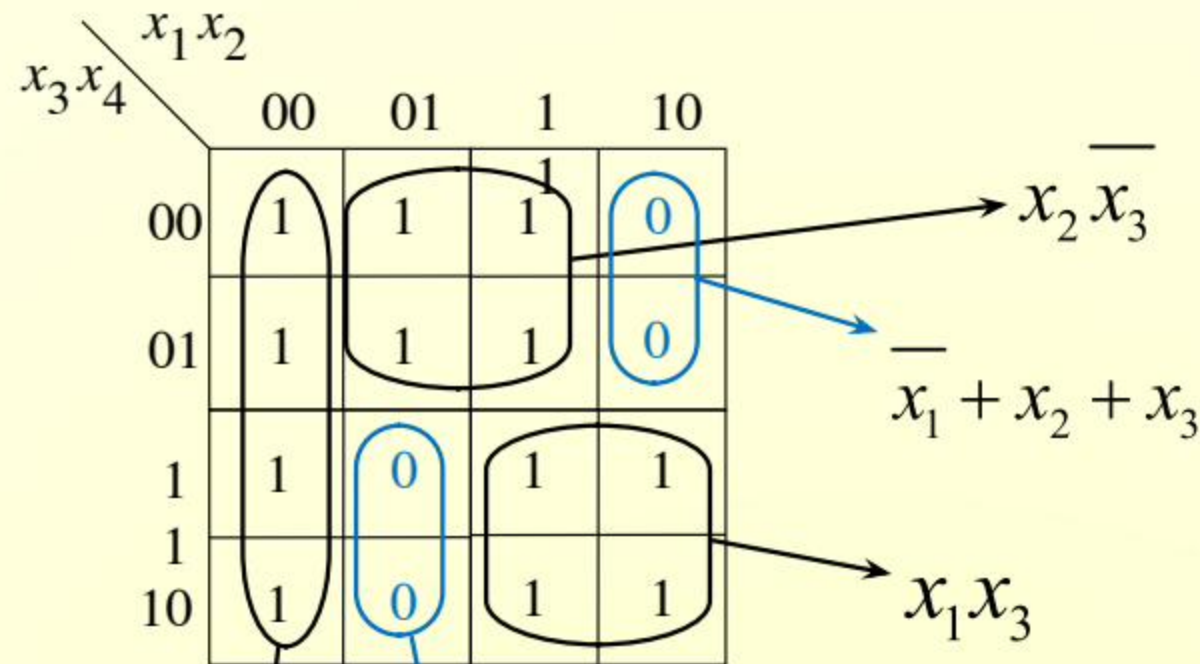1. $F(x_1, x_2, x_3, x_4) = \overline{\overline{x_1 x_2}} + \overline{\overline{x_1 x_3 x_4}} + x_1 x_3 + x_2 \overline{x_3}$



$$F(x_1, x_2, x_3, x_4) = \overline{\overline{x_1 x_2}} + x_2 \overline{x_3} + x_1 x_3$$

$$f = (x_1 + x_2 + x_3)(\overline{x_1} + \overline{x_2} + \overline{x_3})$$

Exercises

$$F(A, B, C) = A\overline{B} + B\overline{C} + \overline{B}C + \overline{A}B$$

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 7, 8, 9, 11, 15)$$

$$F(A, B, C, D) = \prod M(2, 3, 4, 5, 6, 7, 11, 15)$$

2.8 Incompletely Specified functions

- Correspond to circuits where certain input values never occur , which is called *don't care* condition.
- Every corresponding cell is filled with a '*d*'(*don't care-term*)
- Strategy for minimization:
 - Make full use of *ds* as *1s* when minimizing *f* into *SOP*.
 - Make full use of *ds* as *0s* when minimizing *f* into *POS*.

E.g.

:

$x_3x_4 \backslash x_1x_2$					
		00	01	1	10
00	0	1	1	d	0
01	0	1	d		0
1	0	0	d		0
1	1	1	1	d	1
10					

$x_2\bar{x}_3$ (circled in original image)
 $x_3\bar{x}_4$ (circled in original image)

(a) SOP implementation

$x_3x_4 \backslash x_1x_2$					
		00	01	1	10
00	0	1	1	d	0
01	0	1	d		0
1	0	0	d		0
1	1	1	1	d	1
10					

$(x_2 + x_3)$ (circled in original image)
 $(\bar{x}_3 + \bar{x}_4)$ (circled in original image)

(b) POS implementation

Two implementations of
 $f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + d(12, 13, 14, 15).$

Exercises: find the simplest SOP & POS

$$F(A, B, C, D) = \sum m(0, 2, 7, 13, 15) + \sum d(1, 3, 4, 5, 6, 8, 10)$$

$$F(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 8, 10, 11) + \sum d(14, 15)$$


2.9 Cost

- A Function has different implementations(SOP, POS...).
- Which one entails the minimum cost?
- What is the cost?
 - Number of gates plus the total number of inputs(wires) to all gates.
 - Assumption: Single variable in true and complemented forms is at equal cost.

E.g. of cost calculation

Count the cost of $f = x_1 \overline{x_2} + x_3 \overline{x_4}$


1. Draw the circuit diagram:

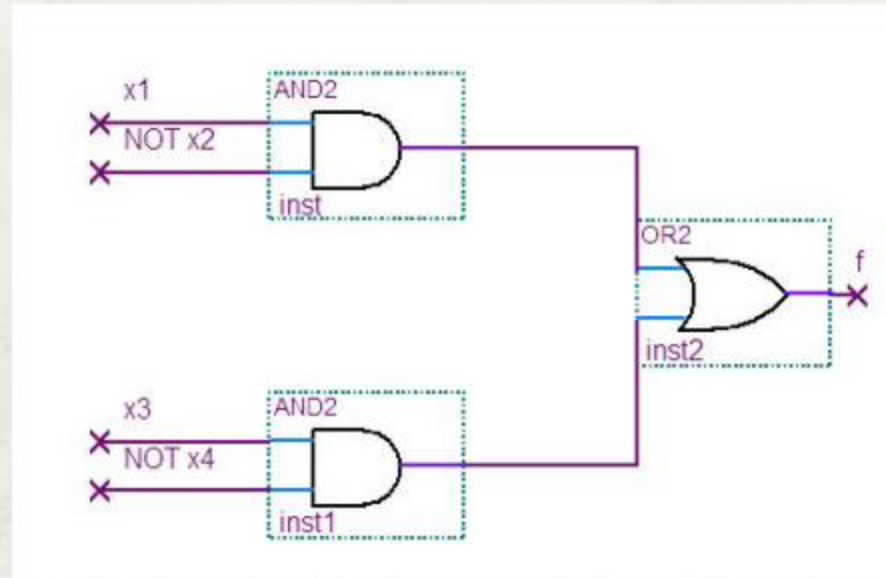


2. 3 gates plus 6 inputs(wires) to all gates entails cost of 9

E.g. of cost calculation (cont.): Minimum cost SOP or POS?


A K-map

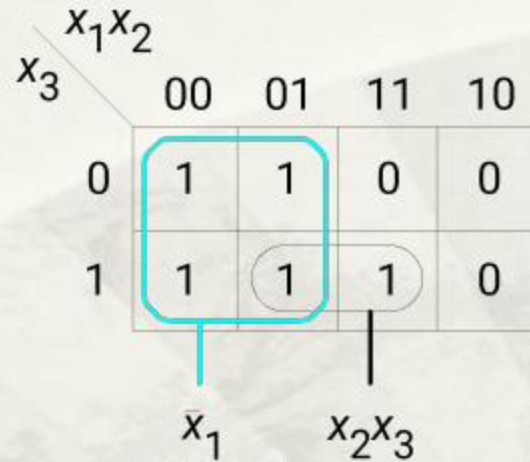

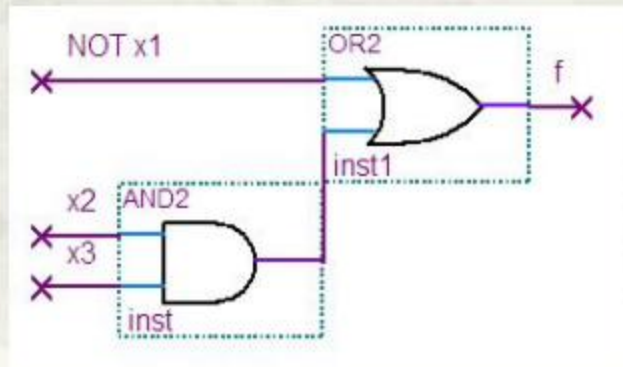
Min-cost SOP: $F(x_1, x_2, x_3) = \bar{x}_1 + x_2x_3$



2 gates + 4 wires = 6

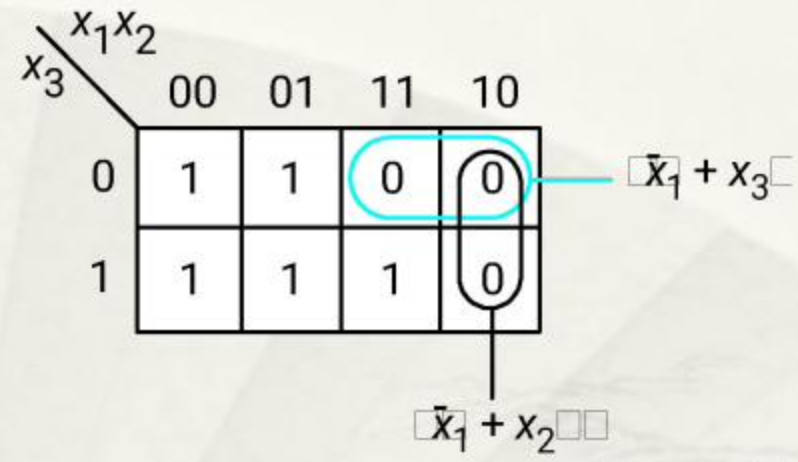

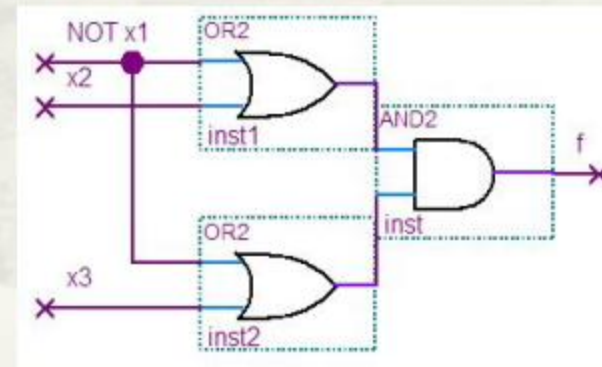Min-cost POS: $F(x_1, x_2, x_3) = (\bar{x}_1 + x_2)(\bar{x}_1 + x_3)$






3 gates + 6 wires = 9


Which one is
better?

E.g. of cost calculation (cont.): Minimum cost SOP or POS?

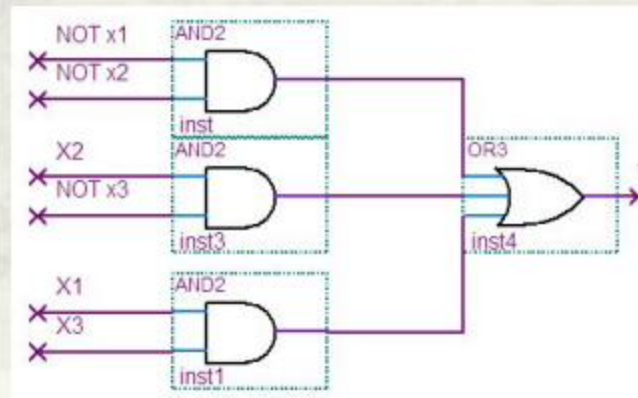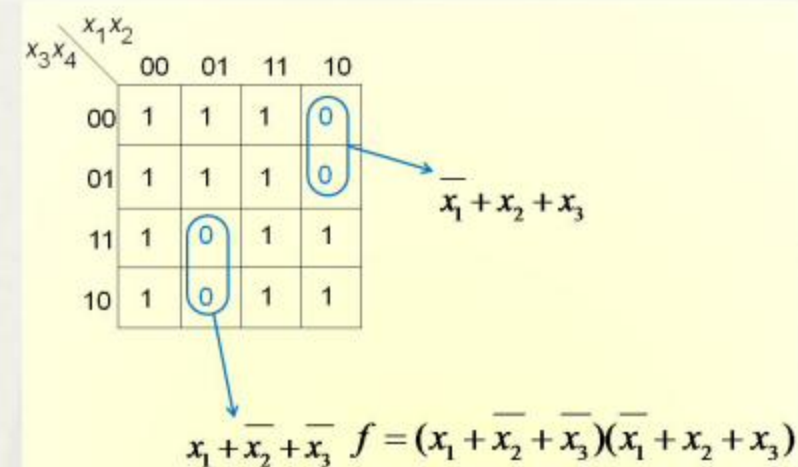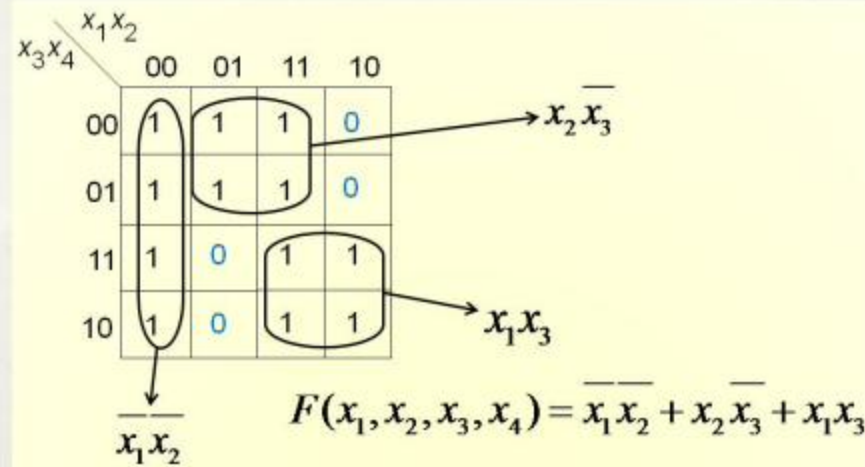□ A previous function: $F(x_1, x_2, x_3, x_4) = \overline{x_1}x_2 + x_1x_3x_4 + x_1x_3 + x_2x_3$



4 gates + 9 wires = 13

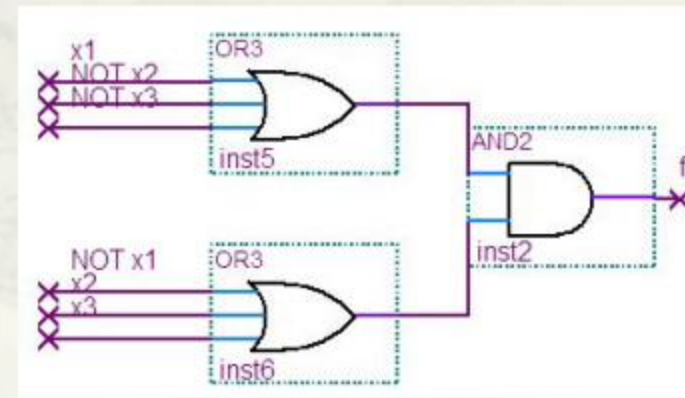

3 gates + 8 wires = 11

Which one is better?

2.10 Multiple-Output functions

- A **group** of functions with sharing variables correspond to a multiple-output circuit.
- The whole system is not usually at minimum cost if simplifying each function separately.

E.g. 1:

$x_3x_4 \backslash x_1x_2$					
		00	01	1	10
00				1	1
01			1	1	1
1	1	1			
10	1	1			

(a) Function f_1

$$f_1 = x_1 \bar{x}_3 + \bar{x}_1 x_3 + x_2 \bar{x}_3 x_4$$

$x_3x_4 \backslash x_1x_2$					
		00	01	1	10
00				1	1
01				1	1
1	1	1	1		
10	1	1			

(b) Function f_2

$$f_2 = x_1 \bar{x}_3 + \bar{x}_1 x_3 + x_2 x_3 x_4$$


In separate design:

Total cost: 14+14=28

Consider sharing product terms in f_1 and f_2

$$f_1 = \underline{x_1 \bar{x}_3} + \bar{x}_1 \bar{x}_3 + x_2 \bar{x}_3 x_4$$

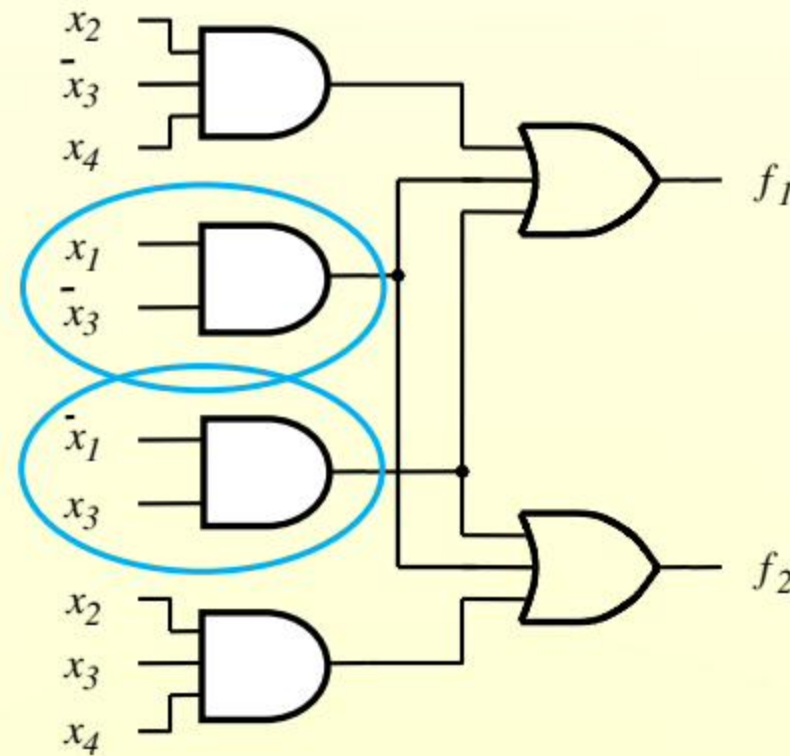
$$f_2 = \underline{x_1 \bar{x}_3} + \bar{x}_1 x_3 + x_2 x_3 x_4$$




(c) Combined circuit f_1 and f_2
for

Integrated cost: $28-6=22$

E.g.
2:

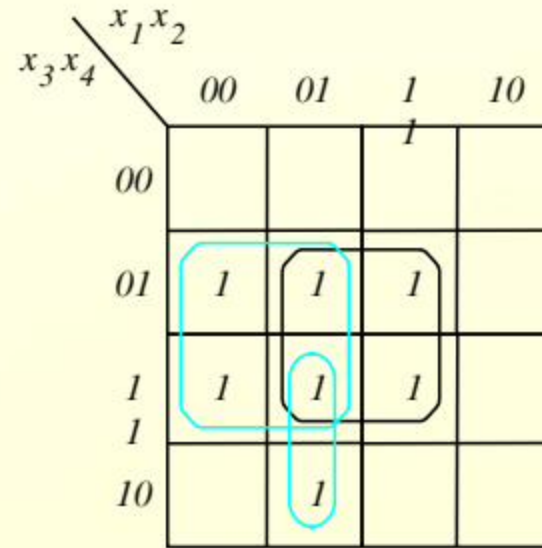

(a) Optimal realization of f_3

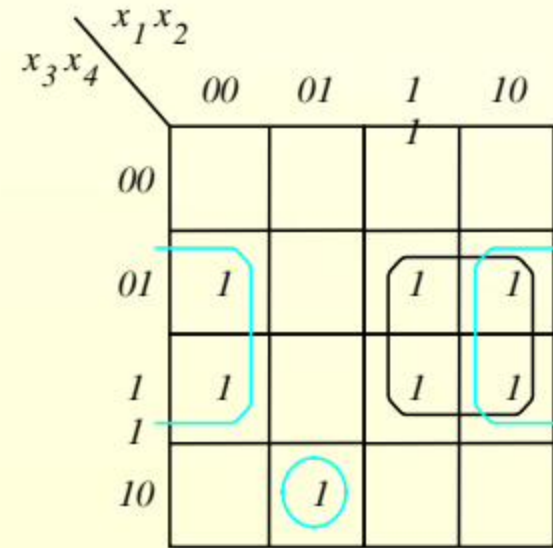

(b) Optimal realization of f_4

$$f_3 = \overline{x_1}x_4 + x_2x_4 + \overline{x_1}x_2x_3$$

$$f_4 = x_1x_4 + \overline{x_2}x_4 + \overline{x_1}x_2x_3\overline{x_4}$$

No sharing
terms!

Cost: 14 + 15 = 29

$x_3 x_4 \backslash x_1 x_2$					
		00	01	1	10
00				1	
01		1	1	1	
1		1	1	1	
10			1		

$x_3 x_4 \backslash x_1 x_2$					
		00	01	1	10
00				1	
01		1		1	1
1		1		1	1
10			1		

(c) Optimal realization of f_3 and f_4 together

Search as many sharing terms!

$$f_3 = \overline{x_1}x_4 + x_1x_2x_4 + \overline{x_1}x_2x_3\overline{x_4}$$

$$f_4 = \overline{x_2}x_4 + x_1x_2x_4 + \overline{x_1}x_2x_3\overline{x_4}$$

Cost: 11+6+6=23

2.11 Concluding Remarks

- ▣ Theorems in Boolean Algebra
- ▣ Manipulation of logic functions
 - ▣ Canonical SOP & POS
 - ▣ Simplest SOP & POS
- ▣ K-map
 - ▣ Structure & features?
 - ▣ How to build it given an arbitrary function?
 - ▣ Principles of simplification?
 - ▣ Special cases...