

CH4 VHDL Language

4.1 What is VHDL?


- VHDL: Very high speed integrated circuits Hardware Description Language.
- An industry standard of IEEE & U.S. DoD used to model digital systems at many levels.
- VHDL 87 & VHDL 93
- A core subset is to be studied.

4.2 Design Units

- Entity
- Architecture
- *Configuration*
- Library
- Package

 4.2.1 Entity Declaration

- Specify the device name and external interfaces.



ENTITY half_adder **IS**

PORT (x, y: **IN BIT**; --signal name, mode & type

s, c: **OUT BIT**);


END half_adder;

-- This is a comment line

4 Modes for VHDL signals

- IN: an input port
- OUT: an output port
- *INOUT*
- *BUFFER: to be detailed in latter chapters.*

Another example

 

ENTITY dec2to4 IS

--a 2-to-4 decoder

PORT(w1,w0,en :IN BIT;

y :OUT BIT_VECTOR(3 DOWNT0 0) --one of array types


);

END dec2to4;

4.2.2 Architecture Body

- Specify the internal details with 1 of following styles:
 - **Dataflow**: A set of concurrent assignment statements.
 - **Behavioral**: A set of sequential assignment statements .
 - **Structural**: A set of interconnected components.

1. Dataflow

 

--E.g.1 : dataflow description of HA

ARCHITECTURE ha_concurrent OF half_adder IS --start of ARC

--Declarative part in between

BEGIN

s <= x XOR y; --2 concurrent signal assignment statements in arbitrary order

c <= x AND y;

END ha_concurrent;

--E.g.2 : dataflow description of dec2to4

**ARCHITECTURE behavior OF dec2to4 IS
BEGIN**


y(0) <= en AND NOT (w(1) OR w(0));

y(1) <= en AND (NOT w(1)) AND w(0);

y(2) <= en AND w(1) AND (NOT w(0));

y(3) <= en AND w(1) AND w(0);

END ha_concurrent;

 

2. Behavioral

- Specify the internal details with a set of statements to be executed **sequentially** encapsulated inside a **process** statement.

--E.g.: behavioral description of 4-to-1 multiplexer

ENTITY mux4to1 IS

PORT(w :IN BIT_VECTOR(3 DOWNT0 0);

s : IN BIT_VECTOR(1 DOWNT0 0);

f: OUT BIT);

END mux4to1;

ARCHITECTURE behave OF mux4to1 IS

BEGIN

PROCESS(s, w) --process statement followed by a sensitivity list

BEGIN --any time an event on any of signals in the list triggers the process

CASE s IS


WHEN "00" =>f<=w(0); --sequential signal assignment statement

WHEN "01" =>f<=w(1);

WHEN "10" =>f<=w(2);


WHEN "11" =>f<=w(3);

END CASE

 

 3. Structural

- An entity(high level) is described as a set of interconnected components(low level).
 - Every component should be implemented in advance.
 - Declare components in the declarative part of architecture body.
 - Link instantiated components to build the top-level circuit.



--E.g. of structural modeling: implementation of FA using HAs as components

ENTITY full_adder IS

PORT (x,y,cin:IN BIT; --interfaces of FA

sum,carry:OUT BIT);

END full_adder;

ARCHITECTURE f_adder OF full_adder IS

COMPONENT half_adder

--HA has its own entity and architecture having been realized

PORT(a,b:IN BIT;

--copied from the PORT clause in HA's entity declaration

s,c:OUT BIT);

END COMPONENT;

SIGNAL h1_s,h1_c,h2_c:BIT; --internal signals in FA

BEGIN

--2 PORT MAP clauses used to instantiate 2 components

h1:half_adder **PORT MAP**(a=>x, b=>y, s=>h1_s, c=>h1_c); --mappings in parenthesis

4.3 Identifiers

- Case insensitive
- Composed of **letters, digits or ‘_’**
- Beginning with a letter is required.
- Ending with ‘_’ is illegal.
- “**_ _**” is illegal.

4.4 Data Objects

4.4.1. constant declarations

CONSTANT rise_time: **TIME** := 10ns;

CONSTANT bus_width: **INTEGER** := 8;

4.4.2. variable declarations

VARIABLE ctrl_status: **BIT_VECTOR**(10 DOWNT0 0);

VARIABLE sum: **INTEGER RANGE** 0 to 100 := 10;

VARIABLE found, done: **BOOLEAN**;

4.4.3. signal declarations

SIGNAL h1_s,h1_c,h2_c:**BIT**;

SIGNAL data_bus: **BIT_VECTOR**(0 TO 7);

SIGNAL gate_delay: **TIME** := 10 NS;

Note: Interfaces declared in **PORT** clause are signals, where the keyword **SIGNAL** is optional .

Variables **Vs.** Signals

- Signals are global, variables are local.
 - Signals are declared outside subprogram and can be used anywhere in architecture body.
 - Variables can be declared and used **only** inside a subprogram.
- '`<=`' for signals; '`:=`' for variables
- Delayed value assignment for signals, instantaneous one for variables.



```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY xor_sig IS
    PORT (a,b,c: IN std_logic;
          x,y : OUT std_logic);
END xor_sig;
ARCHITECTURE sig_arch OF xor_sig IS
    SIGNAL d:std_logic;
BEGIN
    sig :PROCESS(a,b,c)
    BEGIN
        d<=a;
        x<=c XOR d;
        d<=b;
        y<=c XOR d.
```

Result

x= c XOR b

y= c XOR b

If d is a var
instead:

x= c XOR a



4.5 Operators

Logical	Relational	Arithmetical	Catenation
AND	=	+	&
OR	/=	-	
NOT	<	*	
NAND	<= (also for signal assignment)	/	
NOR	>	**(exponentiation)	
XOR	>=	MOD	
XNOR		REM	
		ABS	

4.6 Data Types

4.6.1 Part of Predefined Data Types

- `BIT(0,1)`
- `BIT_VECTOR` -- predefined array type
- `INTEGER` -- $-(2^{31} - 1) \sim (2^{31} - 1)$
- `BOOLEAN(TRUE, FALSE)`
- `CHARACTER`
- ...

4.6.1 Part of Predefined Data Types(cont.)

▣ **STD_LOGIC** --One of the most frequently used types

```
( 'U', -- Uninitialized
  'X', -- Forcing Unknown
  '0', -- Forcing 0
  '1', -- Forcing 1
  'Z', -- High Impedance
  'W', -- Weak Unknown
  'L', -- Weak 0
  'H', -- Weak 1
  '-' -- Don't care
)
```


4.6.2 User Defined Data Types(self-studying)

- **Enumeration types:** anyone of which has a set of user-defined values consisting of identifiers and character literals.

- **E.g.:**

TYPE bit_logic IS ('0','1','Z','X');

TYPE traffic_light IS (red, green, yellow);

TYPE micro_op IS (load, store, add, sub, mul, div);

4.6.2 User Defined Data Types(cont.)

- **Array types:** consists of elements of the same type.
- **E.g.:**
 - TYPE register IS ARRAY(0 TO 7) OF BIT;**
 - TYPE register_1 IS ARRAY(7 DOWNT0 0) OF BIT;**
 - TYPE rom IS ARRAY(0 TO 7) OF register;**
 - TYPE rom IS ARRAY(0 TO 7,0 TO 7) OF BIT;**
 - TYPE std_logic_vector IS ARRAY(natural range<>)OF std_logic**

4.7 Libraries and Packages

- A library includes packages.
- A package encapsulates a set of related declarations of:
 - types
 - constants
 - functions
 - subcircuits(components)
 - ...

4.7.1 Examples of packages in certain libraries

```
package STANDARD is           --in library STD
type BOOLEAN is (FALSE, TRUE); --enumeration type
type BIT is ('0', '1');
type CHARACTER IS (...);
type INTEGER is range -2147483648 to 2147483647;
type BIT_VECTOR is array (NATURAL range <>) of BIT;
...
end STANDARD;
```


4.7.1 Examples of packages in certain libraries(cont.)

```
PACKAGE std_logic_1164 IS      --in library IEEE
```

```
...
```

```
SUBTYPE std_logic IS resolved std_ulogic;
```

```
TYPE std_logic_vector IS ARRAY ( NATURAL RANGE <>) OF std_logic;
```

```
FUNCTION "and" ( l, r : std_logic_vector ) RETURN std_logic_vector;
```

```
FUNCTION "nand" ( l, r : std_logic_vector ) RETURN std_logic_vector;
```

```
FUNCTION "or" ( l, r : std_logic_vector ) RETURN std_logic_vector;
```

```
FUNCTION "nor" ( l, r : std_logic_vector ) RETURN std_logic_vector;
```

```
FUNCTION "xor" ( l, r : std_logic_vector ) RETURN std_logic_vector;
```

```
FUNCTION "xnor" ( l, r : std_logic_vector ) RETURN std_logic_vector;
```

```
FUNCTION "not" ( l : std_logic_vector ) RETURN std_logic_vector;
```

4.7.2 Declarations of libraries and packages

- Syntax as follows:

LIBRARY library-name;

e.g.: **LIBRARY IEEE;**

USE library-name. package-name. Item ;

e.g.: **USE IEEE.STD_LOGIC_1164.ALL;**

By the way

- Declaration of library STD is implicit.
- Declaration of library IEEE is explicit.

4.8 VHDL statements

4.8.1 Concurrent statements

□ 1. Signal assignment statement

```
ARCHITECTURE ha_concurrent OF half_adder IS  
BEGIN
```

```
    s <= a XOR b;
```

```
    c <= a AND b;
```

```
END ha_concurrent;  
ARCHITECTURE behavior OF dec2to4 IS  
BEGIN
```

```
    y(0) <= en AND NOT (w1 OR w(0));
```

```
    y(1) <= en AND (NOT w(1)) AND w(0);
```

```
    y(2) <= en AND w(1) AND (NOT w(0));
```

```
    y(3) <= en AND w(1) AND w(0);
```

```
END ha_concurrent;
```

2. Conditional signal assignment(when...else clauses)

Syntax:

Target - signal <= [value 1 when condition 1 else]
[value 2 when condition 2 else]

...

ENTITY mux4to1 IS

PORT(w : IN **BIT_VECTOR**(3 DOWNT0 0);

s : IN **BIT_VECTOR**(1 DOWNT0 0);

f: OUT **BIT**);

END mux4to1;

ARCHITECTURE behave OF mux4to1 IS

BEGIN

f<=w(0) when s="00" else

w(1) when s="01" else

w(2) when s="10" else

Note:

- When...else must enumerate all the conditions.
--implement 4-to-1 multiplexer using when-else clauses

Library IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY mux4to1 IS

PORT(w :IN STD_LOGIC_VECTOR(3 DOWNTO 0);

s : IN STD_LOGIC_VECTOR(1 DOWNTO 0);

f: OUT STD_LOGIC);

END mux4to1;

ARCHITECTURE behave OF mux4to1 IS

BEGIN

f<=w(0) when s="00" else

w(1) when s="01" else

w(2) when s="10" else

3. Selected Signal Assignment Statement(with...select)

Syntax:

with expression select *--using all valuations as select conditions*

*target-signal <= value 1 when condition 1,
value 2 when condition 2,*

...

value n when condition n,

*--Implement 4-to-1 multiplexer using with-select clauses
[value n+1 when others];*

ARCHITECTURE behave OF mux4to1 IS

BEGIN

WITH s SELECT

y<=w(0) WHEN "00",
w(1) WHEN "01",
w(2) WHEN "10",
w(3) WHEN "11",
'X' WHEN OTHERS;

END behave;

4.8.2 Sequential statements

□ 1. PROCESS statement

Syntax:

[process-label:]PROCESS[(sensitivity-list)]

[process-item-declarations]

begin

various kinds of sequential-statements

end process [process-label];

BEGIN

PROCESS(a,b)

--process statement followed by a sensitivity list

BEGIN

s <= a XOR b;

-- Statements inside process run sequentially

c <= a AND b;

END PROCESS;

END ha_concurrent;

□ 2. Signal assignment statement

ARCHITECTURE ha_concurrent OF half_adder IS

BEGIN

PROCESS(a,b)

BEGIN

s <= a XOR b;

-- Signal assignment statements inside process are sequential

c <= a AND b;

END PROCESS;

□ 3. Variable assignment statement

END ha_concurrent;

□ 3. IF statement

Syntax:

IF boolean-expression 1 THEN
 sequential-statements

*[**ELSIF** boolean-expression 2 then -- elsif clause; if stmt can have 0 or more elsif clauses.*
 sequential-statements]

...

[ELSE -- else clause.

sequential-statements]
IF statement can only be used in behavioral description!

END IF;

--Implement 4-to-1 multiplexer using IF-ELSE statement

ARCHITECTURE behave OF mux4to1 IS

BEGIN

PROCESS (w, s)

BEGIN

IF s ="00" THEN

f <= w(0) ;

ELSIF s ="01" THEN

f <= w(1) ;

ELSIF s ="10" THEN


f <= w(2) ;

ELSE

f <= w(3) ;

END IF ;

END PROCESS ;

 

□ 4. CASE statement

Syntax:

CASE expression IS

WHEN choice 1 => sequential-statements -- branch #1

WHEN choice 2=> sequential-statements -- branch #2 -- Any number of branches

...

[WHEN OTHERS => sequential-statements] -- last branch if necessary

CASE statement can only be used in behavioral description!

END CASE;

--Implement 4-to-1 multiplexer using CASE statement

ARCHITECTURE behave OF mux4to1 IS

BEGIN

PROCESS(s,w)

BEGIN

CASE s IS

WHEN "00" =>f<=w(0);

WHEN "01" =>f<=w(1);

WHEN "10" =>f<=w(2);

WHEN "11" =>f<=w(3);


END CASE;

END PROCESS;

END behave;

--suppose s is of type BIT

 --here the branch "WHEN OTHERS" is optional



□ 5. LOOP statement

Syntax:

[loop-label :] iteration-scheme LOOP
sequential-statements

END LOOP [loop-label] ;

Syntax of FOR :

*[loop-label :] **FOR** identifier in range LOOP*
sequential-statements

END LOOP [loop-label] ;

Syntax of WHILE :

*[loop-label :] **WHILE** boolean-expression LOOP*
sequential-statements

END LOOP [loop-label] ;

--Types of iteration-schemes

--Type 1 : FOR LOOP

--Type 2 : WHILE LOOP

--E.g. 1 of LOOP statement

...

FACTORIAL := 1; --variable

FOR number in 2 to N loop --number used without explicit declaration

 FACTORIAL := FACTORIAL * NUMBER;

end loop; --number++ implicitly

--E.g. 2 of LOOP statement

...

J:=0;SUM:=10; --variables

WH-LOOP: while J < 20 loop --This loop has a label, WH_LOOP.

 SUM := SUM * 2;

 J:=J+3;

end loop **WH-LOOP;**

4.8.3 A comprehensive example:

Implementation of a 7-majority voting

Library ieee;

Use ieee.std_logic_1164.all;

Use ieee.std_logic_unsigned.all;

Entity vote7 is

port (men: IN std_logic_vector(6 downto 0) ; --let element value 1 $\square$ voting for
Vote_result: OUT std_logic); --let value 1 $\square$ voted through

End vote7;

Architecture vote of vote7 is

signal pass: std_logic;

begin

Process (men)

variable temp :std logic vector(2 downto 0); --set a counter to record votes

begin

temp:="000";

For i in 0 to 6 loop

--loop vars without declarations in advance

if (men(i)='1') then

temp:=temp+1;

end if;

end loop;

pass<=temp(2);

-- determine whether votes reach 4

End Process;

Vote_result<=pass;

-- pass the result to the output interface

End vote;