 


CH5 Basic Storage Units:

Latches, Flip-flops and Counters


5.1 A Brief Introduction

An alarm system



- **'Set'** triggers the alarm.
- The alarm **remains active** even if **Set** = 0.
 - The memory element must **store the state**.
 - The present **On / $\overline{\text{Off}}$** is determined by not only inputs but also the past state.
- The alarm is turned off if **Reset** = 1.

Review: NOR gate & NAND gate

 

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0


NOR's truth table



x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

NAND's truth table

5.2 Basic Latch

 

(a) Circuit

Complements of each other in normal state

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

Anomalous state

(b) Characteristic table


State stored!

When $S = 0$ & $R = 0$, $Q^{n+1} = Q^n$

Q^{n+1} (or $Q(t+1)$): next state

Q^n (or $Q(t)$): present state

More about the anomalous state

 

- What if S and R go back to 0 simultaneously ?
 - Outputs **Oscillate** between 0 & 1
 - Although S and R do not change simultaneously, the next state is not easily predicted.
- Critical to **avoid having both S & R = 1.**

Logic expression

RS					
		00	01	11	10
Q^n	0	0	1	d	0
	1	1	1	d	0


$$Q^{n+1} = S + \overline{R}Q^n$$

Constraint : $RS = 0$

State diagram



- Another type of characteristic table

		RS			
		00	01	11	10
Q^n	0	0	1	d	0
	1	1	1	d	0

 

Timing diagram

  - The basic latch changes its state once there's a change in one of input values which leads to unstability and




S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

Irregularity of waveforms

 
5.2 Gated SR Latch

- An input disturbance may affect the state for a basic latch.
 - State cannot be retained consistently.




- The clock signal allows changes in states to occur at periodic time intervals.

Timing diagram of gated SR latch

 


More regular output Q & Qc

Gated SR with NAND gates

 

5.3 Gated D Latch

 


- A gated SR latch in essence.
- 1 input D
- S & R are always complements of each other.


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

$Q^{n+1} = D$

(b) Characteristic table

 

(c) Graphical symbol


 


(d) Timing diagram

Basic SR, gated SR and gated D are all level sensitive!


5.4 Master-Slave and Edge-Triggered D

Flip-flop

  


- Q_m doesn't change when Clock=0
- Q_s(Q) doesn't change when Clock=1
- Q changes **only when** Clock changes from 1 to 0(**falling edge**)
- **Flip-flop: an edge-triggered storage element that changes its output state only at the edge of Clock.**

Timing diagram

 


A different edge-triggered Dff

And then

 


In turn


A different edge-triggered Dff

 

 
Suppose **D=0** and D changes from 0 $\rightarrow$ 1 during Clk=1



 
Suppose **D=0** and D changes from 0 $\rightarrow$ 1 during Clk=1



 Suppose **D=1** and D changes from 1 $\rightarrow$ 0 during Clk=1




 Suppose **D=1** and D changes from 1 $\rightarrow$ 0 during Clk=1




Q is retained regardless of changes of D! $\longrightarrow$ **Edge triggered!**


A different edge-triggered Dff

 

Edge-triggered principle

 


A different edge-triggered Dff


 


Edge-triggered principle

 Level sensitive Vs. Edge-triggered storage element





D flip-flop with Clear and Preset

  


- Active low.
- **Asynchronous** Clear and Preset.
- Falling-edge triggered

  A rising-edge triggered Dff with Clear & Preset



5.5 T Flip-flop


 


T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$


(b) Truth table

$$Q^{n+1} = T\bar{Q}^n + \bar{T}Q^n$$

Toggle flip-flop

  

5.6 JK Flip-flop

 


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

$$Q^{n+1} = J\bar{Q}^n + \bar{K}Q^n$$

Toggle flip-flop

 

(c) Graphical symbol

5.7 Synchronous Counters

- ▣ Counting
- ▣ Timing
- ▣ Generating controlling signals(e.g. clock)
- ▣ Usually consisting of **toggle flip-flops**

Understanding Counters' behavior

- A flip-flop stores 1-bit state **stably**.
- An **n-bit(modulo- 2^n)** counter consists of **n** flip-flops synchronized by a public clock.
- Counting sequence is formed by simultaneously toggling 1 or more flip-flop in a counter controlled by the public clock.

5.7.1 Counting behavior

- A 3-bit(modulo-8) up-counter

<i>Clock cycle</i>	<i>Q₂</i>	<i>Q₁</i>	<i>Q₀</i>
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q₁ changes

Q₂ changes

A single Clk signal

Number of flip-flops?

Types of ff to be used?

E.g.: T(or JK) flip-flops!

5.7.2 Implementation of an n-bit up-counter

□ A 3-bit up-counter(modulo-8)

Clock cycle	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q₁ changes

Q₂ changes

How?

Q₀ toggles in each Clk cycle

Q₁ toggles after Q₀=1

Q₂ toggles after Q₀=1 & Q₁=1

And it follows that:

For an **n-bit** up counter(modulo-2ⁿ)
Q_{n-1} toggles after Q₀~Q_{n-2} are all 1s!

Implement an n-bit up-counter

$Q^{n+1} = T\overline{Q^n} + \overline{T}Q^n$ when $T = 1$, it toggles its state.

Consider Q_0 which toggles in every Clk cycle $\rightarrow \underline{T_0 = 1}$

Consider Q_1 which toggles if $Q_0 = 1 \rightarrow \underline{T_1 = Q_0}$

Consider Q_2 which toggles if $Q_1 = 1 \& Q_0 = 1 \rightarrow \underline{T_2 = Q_1Q_0}$


Consider Q_3 which toggles if $Q_2 = 1 \& Q_1 = 1 \& Q_0 = 1 \rightarrow \underline{T_3 = Q_2Q_1Q_0}$

...


and it follows that :

Q_n toggles if $Q_{n-1} = 1 \& \dots \& Q_1 = 1 \& Q_0 = 1 \rightarrow \underline{T_n = Q_{n-1}Q_{n-2}\dots Q_1}$

 5.7.3 A 4-bit(modulo-16) counter with T flip-flops




(a) Circuit

 


(b) Timing diagram

5.7.4 Enable and Clear Capability

 

- When Enable=0, the counting process is paused
- When Clear=0(active low), the counter is reset to all 0s
- Enable is synchronized by clock, while Clear is not(Asynchronization)!

5.7.5 A 4-bit counter with D flip-flops

 


5.7.6 Counters with **parallel load**

- Unnecessary to count from 0
- Desirable to start with any value count.

When **load=0**, the counting process goes on if Enabled.



When **load=1**, $D_3 \sim D_0$ are selected and loaded into the counter when next rising edge of Clock occurs.

 In this case, the counter is reset to $D_3 D_2 D_1 D_0$ and counts from it.



  5.7.7 Implementation of any modulo-N counter



- An n-bit up-counter functions as a modulo- 2^n .
- Desirable to implement a modulo-N ($N < 2^n$) counter.
- Skip some(?) counts from the modulo- 2^n counting sequence by
 - linking some outputs to the load input so as to reset the counter to “ $D_{n-1}...D_0$ ” before it counts to all 1s.



Modulo-? and other ways out?

  5.7.7 Implementation of any modulo-N counter


- An n-bit up-counter functions as a **modulo- 2^n** .
- Desirable to implement a **modulo-N ($N < 2^n$)** counter.
- **Skip some(?) counts** from the modulo- 2^n counting sequence **by**
 - linking some outputs to the **load** input so as to reset the counter to " $D_{n-1}...D_0$ " before it counts to all 1s.



Modulo-6 counter


Modulo-10 counter(BCD counter)

 - Based on a 4-bit counter(modulo-16) with reset synchronization.




Modulo-10 counter with carry out


- Used to create a counter modulo a base with larger value.
- Carry=1 when Q=9

 

Exercise 1:

 


Exercise 2:

 

What if $N > 2^n$?

 - ▢ modulo-(N ?) counter
 - ▢ Cascading 2 BCD counters




1. Synchronous system
2. Without loading
3. Left counter works in every clock cycle
4. Right one is driven by the Carry of the left one.
5. **What's** the ratio of counting frequency between the two?
6. The Carry out is generated every ? clock cycles.
7. **Range of counts as a whole?**

 Question: Modulo what base if cascading a **modulo-A** counter and a **modulo-B** counter?
And how about cascading more counters?

What if $N > 2^n$

- Implementation of a **modulo-N** counter, $N \neq A * B$
 - Achieved by cascading 2 BCD counters with **integral parallel load**



counter

1. Synchronous system

2. **Loads enabled simultaneously.**

3. **Note the inputs of the AND gate!**

4. Counts from **00~23(2 BCD groups).**

Question: How to implement other modulo-X counter? E.g.: modulo-60?

5.7.8 Modulo-X counters in QUARTUS II


□ **E.g.:** The modulo-10 counter

1. Name: **74160**. (**74161** as the 4-bit up counter)

2. LDN(Load) is **active low**.


3. ENT & ENP (Enable), RCO(Carry).

4. D~A(D3~D0), QD~QA(Q3~Q0)

 


5.7.8 Modulo-X counters in QUARTUS II

- The modulo-24 counter with 74160s

 


Signal correspondence by name

Simulation result

 

Exercise 3:

 

What if both counters are replaced with 2 BCD counters?

5.8 Storage elements in VHDL

5.8.1 Code for the gated D latch


```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY Dlatch IS
    PORT ( D, Clk : IN STD LOGIC ;
          Q : OUT STD LOGIC) ;
END Dlatch ;
ARCHITECTURE Behavior OF Dlatch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

--D latch as a example

-- D or Clk can cause an output change!


-- level sensitive

-- implied memory

 

 
5.8.2 Code for the D flip-flop

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY D_ff IS
    PORT ( D, Clk : IN STD LOGIC ; --D flip-flop as a example
          Q : OUT STD LOGIC) ;
END D_ff;
ARCHITECTURE Behavior OF D_ff IS
BEGIN
    PROCESS ( Clk )                --Only active edge can cause an output change
    BEGIN
        IF Clk'EVENT AND Clk ='1' THEN --rising edge triggered
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



Code for the Dff with asynchronous clear
 
```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY DFF IS
    PORT ( D, Clk, Clr : IN STD LOGIC ;
          Q : OUT STD LOGIC) ;
END DFF;
ARCHITECTURE Behavior OF DFF IS
BEGIN
    PROCESS ( Clk, Clr )
    BEGIN
        IF Clr = '0' THEN
            Q <= '0';
        ELSIF Clk'EVENT AND Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```




--Clear signal NOT clocked

--Clear signal NOT clocked

 5.8.3 Code for a counter

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, Clr, En: IN STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)) ;
END upcount ;
ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Clr )
    BEGIN
        IF Clr = '0' THEN
            Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF En = '1' THEN
                Count <= Count + 1 ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```



--a 4-bit up counter as an example
--with clear & enable capability

--internal signal

--asynchronous clear

--synchronous enable

-- The Count signal passes the result to Q outside of the clock process

Alternative code

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, Clr, En: IN STD_LOGIC ;
          Q : BUFFER STD_LOGIC_VECTOR (3 DOWNT0 0)) ;    -- the BUFFER mode
END upcount ;
ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS ( Clock, Clr )
    BEGIN
        IF Clr = '0' THEN
            Q <= "0000" ;
        ELSIF (Clock'EVENT AND Clock ='1') THEN
            IF En = '1' THEN
                Q <= Q+1 ;                                --Q is directly used as being of the mode BUFFER
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;
```


Code for a counter with parallel load

...

ENTITY upcount IS

PORT (Data : IN STD_LOGIC_VECTOR(3 downto 0) ; --parallel data inputs

 Clock, Clear, Ld : IN STD LOGIC ;

 Q : BUFFER STD_LOGIC_VECTOR(3 downto 0)) ;

END upcount ;

ARCHITECTURE Behavior OF upcount IS

BEGIN

 PROCESS (Clock, Clear)

 BEGIN

 IF Clear= '0' THEN

 Q <= "0000" ;

 ELSIF (Clock'EVENT AND Clock = '1') THEN

 IF Ld = '1' THEN --parallel load(active high)

 Q <= Data ;

 ELSE

 Q <= Q + 1 ;

 END IF;

 END IF;

 END PROCESS;

END Behavior;

Code for a modulo-N counter

-- with 74160 counter as the example

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
USE ieee.std_logic_unsigned.ALL;
```

```
entity T74LS160 is
```

```
    Port ( Clk : in  std_logic;
```

```
          Q : buffer std_logic_vector(3 downto 0);  --QD,QC,QB,QA
```

```
          Carry : out std_logic;
```

```
          Clr : in  std_logic;
```


```
          Data : in  std_logic_vector(3 downto 0);  --D,C,B,A
```

```
          Ld : in  std_logic;                        --active low
```

```
          p : in  std_logic;                         --ENP
```

```
          t : in  std_logic);                       --ENT
```

```
end T74LS160;
```

 

architecture BEHAVIORAL of T74LS160 is

begin

Carry<='1' when (Q="1001" and t='1' and Clr='1') else '0';

process(clk,clr)

begin

if Clr='0' then Q<="0000";

elsif(rising_edge(clk)) then

if(ld='1') then

if(p='1') then

if(t='1') then

if(Q="1001")

Q<="0000";

else Q<=Q+1;

end if;

else Q<=Q;

end if;

--asynchronous clear

--the rising_edge function

--active low

--modulo-10 counter

--state kept if t=0

```
        else Q<=Q;           --state kept if p=0
    end if;
    else Q<=Data;           --parallel load(active low)
    end if;
end if;
end process;
end BEHAVIORAL;
```