 


CH6 Synchronous Sequential Logic Circuits

6.1 A general structure



- ▣ Outputs may depend on both inputs & present states of flip-flops.
 - ▣ **External(Primary) outputs**(e.g.: Z)
 - ▣ **Internal outputs**: inputs of flip-flops(D, T, JK...).
- ▣ **Inputs:**
 - ▣ **External(primary) inputs**(e.g.: W)
 - ▣ **Internal inputs**: feedback inputs from flip-flops(present state).

Moore type & Mealy type

- **Moore type**: whose external outputs **only** depend on the present state.
- **Mealy type**: whose external outputs depend on **both** the present state and primary inputs.

6.2 Basic Design Steps

- **Implementation of a “11” sequence detector:**
 - A primary input w , and an output, z .
 - **Serial** input and output synchronized by clock signal.
 - A single clk synchronizing rising edge triggered ffs.
 - $Z=1$ if $w=1$ during two or more consecutive clock cycles; $z=0$ otherwise.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

6.2.1 State diagram

Clockcycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
w:	0	1	0	1	1	0	1	1	1	0	1
z:	0	0	0	0	0	1	0	0	1	1	0

- Determine number of states needed.
 - **Set a starting state** in the first place.
 - Consider state transitions from the starting state to the last, which covers all the cases.

Assume **A** is the initial state: w=0 at the beginning; z=0

Assume **B** is the 2nd state: the 1st '1' occurs at the input; z=0


Assume **C** is the 3rd state: the 2nd '1' occurs at the input; **z=1**

Z is determined only by the state!

Moore type


State diagram: the graphical representation

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Step-by-step derivation of the state diagram

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 

6.2.2 State table

 

State diagram

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

State table

6.2.3 State assignment

- Letter states in the table.
- Binary states in flip-flops.
- Each of letters should be assigned a binary value.
- **Consider:**

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

How many flip-flops at least? **2**

2 state variables(**assume: y_1 & y_0**) correspond to 2 flip-flops.

00 01 10 11

Choose 3 of them!

More than one assignment!

Choose one of assignments arbitrarily

- Let $A=00$, $B=01$, $C=10$, value of 11 not used.

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1



Present state	Next state		Output z
	$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	
A	00	01	0
B	01	10	0
C	10	10	1
	11	dd	d

Binary state table

6.2.4 Derivation of Next-state & Output expressions

- A slight modification on the state table.

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

Before modification

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
	11	dd	dd	d
C	10	00	10	1

After modification

What's the difference?

A combination of K-maps

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
	11	<i>dd</i>	<i>dd</i>	<i>d</i>
C	10	00	10	1

Present state $y_2 y_1$	Next state	
	$w = 0$	$w = 1$
	Y_2	Y_2
00	0	0
01	0	1
11	<i>d</i>	<i>d</i>
10	0	1

$$Y_2 = wy_1 + wy_2$$

Present state $y_2 y_1$	Next state	
	$w = 0$	$w = 1$
	Y_1	Y_1
00	0	1
01	0	0
11	<i>d</i>	<i>d</i>
10	0	0

$$Y_1 = \overline{w} \overline{y_1} y_2$$

		y_1	
		0	1
y_2	0	0	0
	1	1	<i>d</i>

$$z = y_2$$

Choice of flip-flops

- D? T? JK?
- E.g.: choose D flip-flops.
- Consider D's output expression $Q^{n+1} = D$

$$Y_2 = wy_1 + wy_2$$



$$D_2 = Y_2 = wy_1 + wy_2$$



$$Y_1 = w\overline{y_1}\overline{y_2}$$




$$D_1 = Y_1 = w\overline{y_1}\overline{y_2}$$




Internal outputs(excitation functions)

6.2.5 Build the circuit diagram

 



6.2.6 The timing diagram

 

6.2.7 Some detailed issues

  1. Set the starting state

- The circuit can start with any state: 00, 01, 10 or **11**
- Setting “00” as the initial state is a good way.



2. The potential impact of unused states

- The “11” state is not used during the derivation of state diagrams.
- However, it may occur typically during the startup.
- It's necessary to check the behavior of the circuit once it's in the “11” state.

$$Y_2 = wy_1 + wy_2 \quad Y_1 = w\overline{y_1}\overline{y_2} \quad z = y_2$$

Substituting $y_2 = 1$ and $y_1 = 1$ to equations above gives :

$$Y_2 = w \quad Y_1 = 0 \quad z = 1$$

Which indicates :

The circuit changes its state to "00" if $w = 0$

The circuit changes its state to "10" if $w = 1$



Self-restoring!

The capability of automatically entering any valid state.

3. State-assignment problem

- A state table corresponds to more than one assignment.
- Consider another one:
 - State A, B, **C** are represented with valuations $y_2y_1=00, 01$, and **11** respectively

	Present state y_2y_1	Next state		Output z	Output z
		$w = 0$	$w = 1$		
		Y_2Y_1	Y_2Y_1		
A	00	00	01	0	0
B	01	00	11	0	0
C	11	00	11	1	1
	10	dd	dd	d	d

$$Y_1 = D_1 = w$$

$$Y_2 = D_2 = wy_1$$


$$z = y_2$$


$$Y_2 = wy_1 + wy_2$$

$$Y_1 = w\overline{y_1y_2}$$

$$z = y_2$$

The corresponding circuit

 

 

4. Selecting other flip-flops

- How about JK flip-flop?



6.2.8 Summary of Design Steps

- Derive the state diagram by setting an initial state.
- State diagram □ state table.
- *State minimization* □ *optimal state table*.
- State assignment.
- Deriving next-state functions and external output functions
- Choice of flip-flops.
- Deriving excitation functions(D,J,K,T...).
- Build the circuit diagram.
- Analysis of impact of unused states.

6.3 Mealy Type Implementation


- Implementation of a “11” sequence detector:
 - A primary input w , and an output, z .
 - Rising edge triggered.
 - $Z=1$ if $w=1$ during two or more consecutive clock cycles; $z=0$ otherwise.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0


6.3.1 State diagram

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

 

- Z is determined by both the inputs and the present state.

6.3.2 State table

 

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

6.3.3 State assignment

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1



Only 1 flip-flop is needed.

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1


6.3.4 Derivation of Next-state & Output expressions

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1


$$Y = D = w$$

$$z = wy$$

6.3.5 Circuit & timing diagram

 

(a) Circuit

 

(b) Timing diagram


6.5 Another example(Mealy Type)

- Implementation of a vending coffee machine:
 - ¥1.5 for each cup.
 - Either a 50 cent coin or a ¥1 coin is accepted.
 - Sell a coffee If ¥1.5 deposited, or return ¥ 0.5 change besides sending out a coffee if ¥ 2 deposited.
- Considerations:
 - Which inputs and what do they represent?
 - Which outputs and what do they represent?
 - State changes?

6.5.1 State diagram

- Determine number of primary inputs and external outputs.
 - Set an input **A**: deposit a ¥1 coin or not.
 - Set an input **B**: deposit a ¥0.5 coin or not.
 - Set an output **Y**: sell a cup of coffee or not.
 - Set an output **Z**: return a ¥0.5 change or not.
- Set a starting state **S0**
- Set the 2nd state **S1**: a ¥0.5 coin is deposited.
- Set the 3rd state **S2**: a ¥1 coin is deposited.
- **S0 is the final state as well!**


6.5.1 State diagram

 

AB=11 never occurs

Mealy state diagram

6.5.2 State table

 

Q	AB			
	00	01	11	10
S_0	$S_0/00$	$S_1/00$	d/dd	$S_2/00$
S_1	$S_1/00$	$S_2/00$	d/dd	$S_0/10$
S_2	$S_2/00$	$S_0/10$	d/dd	$S_0/11$

6.5.3 State assignment

Let $S0 = 00$, $S1 = 01$, $S2 = 10$, 11 left unused.

AB		00	01	11	10
Q ₁ Q ₀	00	00/00	01/00	dd/dd	10/00
	01	01/00	10/00	dd/dd	00/10
	11	dd/dd	dd/dd	dd/dd	dd/dd
	10	10/00	00/10	dd/dd	00/11

Q1&Q0 as state variables

6.5.4 Finding expressions for outputs

Q ₁ Q ₀ \ AB		AB			
		00	01	11	10
Q ₁ Q ₀	00	00/00	01/00	dd/dd	10/00
	01	01/00	10/00	dd/dd	00/10
	11	dd/dd	dd/dd	dd/dd	dd/dd
	10	10/00	00/10	dd/dd	00/11

$$D_1 = Q_1 \bar{A} \bar{B} + \bar{Q}_1 \bar{Q}_0 A + Q_0 B$$

$$D_0 = \bar{Q}_1 \bar{Q}_0 B + Q_0 \bar{A} \bar{B}$$

$$Y = Q_1 B + Q_1 A + Q_0 A$$

$$Z = Q_1 A$$

Implication of using Dffs

Q ₁ Q ₀ \ AB		AB			
		00	01	11	10
Q ₁ Q ₀	00	0	0	d	1
	01	0	1	d	0
	11	d	d	d	d
	10	1	0	d	0

$$D_1 = Q_1 \bar{A} \bar{B} + \bar{Q}_1 \bar{Q}_0 A + Q_0 B$$

Q ₁ Q ₀ \ AB		AB			
		00	01	11	10
Q ₁ Q ₀	00	0	1	d	0
	01	1	0	d	0
	11	d	d	d	d
	10	0	0	d	0

$$D_0 = \bar{Q}_1 \bar{Q}_0 B + Q_0 \bar{A} \bar{B}$$


Q ₁ Q ₀ \ AB		AB			
		00	01	11	10
Q ₁ Q ₀	00	0	0	d	0
	01	0	0	d	1
	11	d	d	d	d
	10	0	1	d	1

$$Y = Q_1 B + Q_1 A + Q_0 A$$

Q ₁ Q ₀ \ AB		AB			
		00	01	11	10
Q ₁ Q ₀	00	0	0	d	0
	01	0	0	d	0
	11	d	d	d	d
	10	0	0	d	1

$$Z = Q_1 A$$

6.5.5 The circuit

 

6.5.6 The impact of the state “11”

- Substitute $Q1Q0=11$ into

$$D1 = Q1\bar{A}\bar{B} + \bar{Q}1\bar{Q}0A + Q0B$$

$$D0 = \bar{Q}1\bar{Q}0B + Q0\bar{A}\bar{B}$$

$$Y = Q1B + Q1A + Q0A$$


$$Z = Q1A$$

$$D1 = Q1^{n+1} = \bar{A} + B$$

$$D0 = Q0^{n+1} = \bar{A}\bar{B}$$

$$Y = A + B$$

$$Z = A$$

 

Anything wrong?


1. Incapable of self-restoring.
2. Errors in charging.

Resetting when power-on is required.

 6.4 Implementation in VHDL

--Code for Moore type implementation


```
1  LIBRARY ieee ;  
2  USE ieee.std_logic_1164.all ;  
3  ENTITY simple IS  
4    PORT ( Clock, Resetn, w : IN STD_LOGIC ;  
           z : OUT STD_LOGIC ) ;  
5  END simple ;  
  
7  ARCHITECTURE Behavior OF simple IS  
8    TYPE State_type IS (A, B, C) ;  
9    SIGNAL y : State_type ;  
10 BEGIN
```



```

13  IF Resetn = '0' THEN
14      y <= A ;
15  ELSIF (Clock'EVENT AND Clock = '1') THEN
16      CASE y IS
17          WHEN A =>
18              IF w = '0' THEN
19                  y <= A ;
20              ELSE
21                  y <= B ;
22              END IF ;
23          WHEN B =>
24              IF w = '0' THEN
25                  y <= A ;
26              ELSE
27                  y <= C ;
28              END IF ;
29          WHEN C =>
30              IF w = '0' THEN
31                  y <= A ;
32              ELSE
33                  y <= C ;
34              END IF ;
35          END CASE ;
36      END IF ;
37  END PROCESS ;
38  z <= '1' WHEN y = C ELSE '0' ;
39  END Behavior ;

```

 

--WHEN OTHERS not required

--Code for Mealy type implementation

LIBRARY ieee ;

USE ieee.std_logic_1164.all ;

ENTITY mealy IS

PORT (Clock, Resetn, w : IN STD_LOGIC ;
z : OUT STD_

END mealy ;

ARCHITECTURE Behavior OF mealy IS

TYPE State_type IS (A, B) ;

SIGNAL y : State_type ;



BEGIN

PROCESS (Resetn, Clock)

BEGIN

IF Resetn = '0' THEN

y <= A ;

  

ELSIF (Clock'EVENT AND Clock = '1') THEN

CASE y IS

WHEN A =>

IF w = '0' THEN

y <= A ;

ELSE

y <= B ;

END IF ;

WHEN B =>

IF w = '0' THEN y <= A ;


ELSE y <= B ;

END IF ;

END CASE ;

END IF ;

END PROCESS ;

 

PROCESS (y, w)

BEGIN

CASE y IS

WHEN A =>

z <= '0' ;

WHEN B =>

z <= w ;

END CASE ;

END PROCESS ;

END Behavior ;

